

Ferrite Core Antenna Transformer Efficiency

- Characteristics
- Measurements
- Some Observations

Dan Koellen
AI6XG

Today's Adventure

- You Will Learn:
 - a Bit About Me
 - What is Different About Ferrite Cores
 - How This Affects Transformers
 - Two Methods to Measure Transformer Efficiency/Loss
 - What Affects Transformer Loss Measurements
- And You Will See:
 - Examples of Transformer Loss Measurements
 - Nice Photos From Mountain Summits

AI6XG

- First Licensed in 1973
 - License Lapsed in late 1980s
 - New Ticket in 2017
 - Thank you Bay Area Maker Faire!
- Primary Operation is HF CW
 - Summits on the Air (SOTA)

What is Summits On The Air?

- Operation from Mountain Tops
 - Pack in equipment
 - Portable power
 - QRP Radios



SOTA Antennas

- Lightweight
- Compact
- Efficient
- Easy to Assemble in Varying Conditions and Environments



Below and Above Tree Line



Anytime of the Year



Courtesy of KE6MT

End Fed Half Wave (EFHW)

- Popular SOTA Antenna
- Lightweight and Compact



End Fed Half Wave (EFHW)


- Several Configurations
 - Sloper
 - Inverted Vee
 - Inverted L

End Fed Half Wave (EFHW)

- Multiband
- Resonant
- No Tuner Required




EFHW Transformer

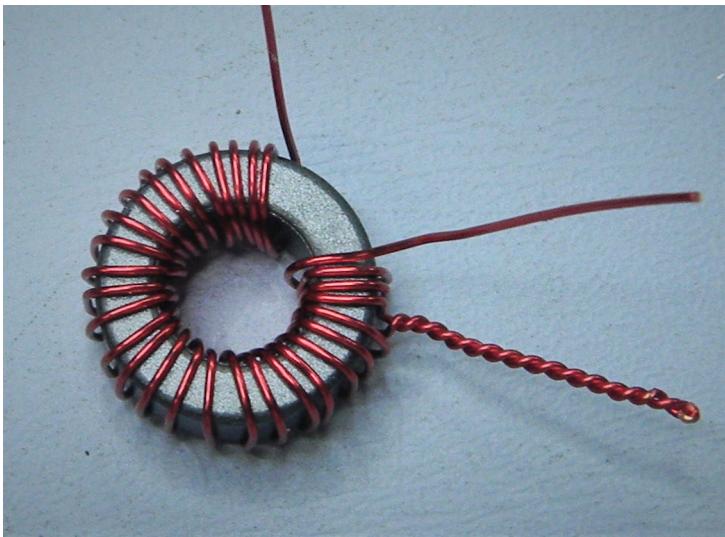

- Transform from High Z at Feedpoint
 - 49:1, 64:1, 81:1
- Ferrite Core Used
- Insertion Loss
 - Am I Losing Power?
 - Measured with VNA S21
 - nanoVNA


EFHW Transformer

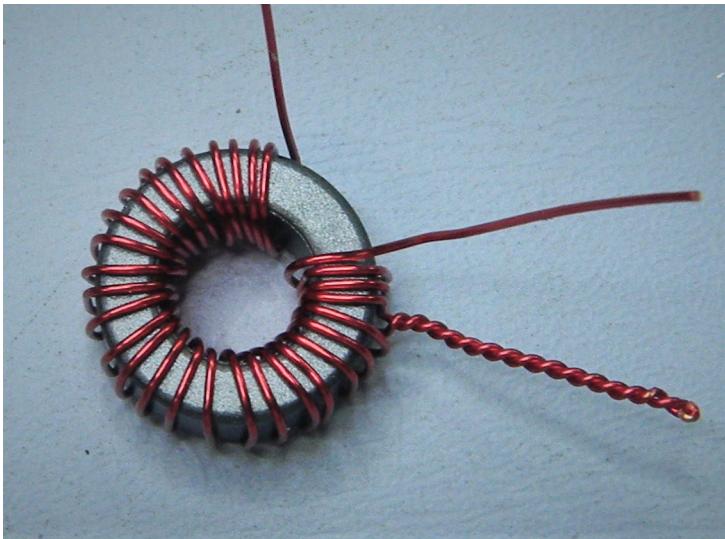

- Why use a Ferrite Core?
 - High Permeability
 - Wide Bandwidth
 - Powered Iron Cores Not Used
- Which Cores Are Used?
 - FT50-43 toroid popular for QRP
 - FT240-43 toroid popular for QRO


Complex Permeability

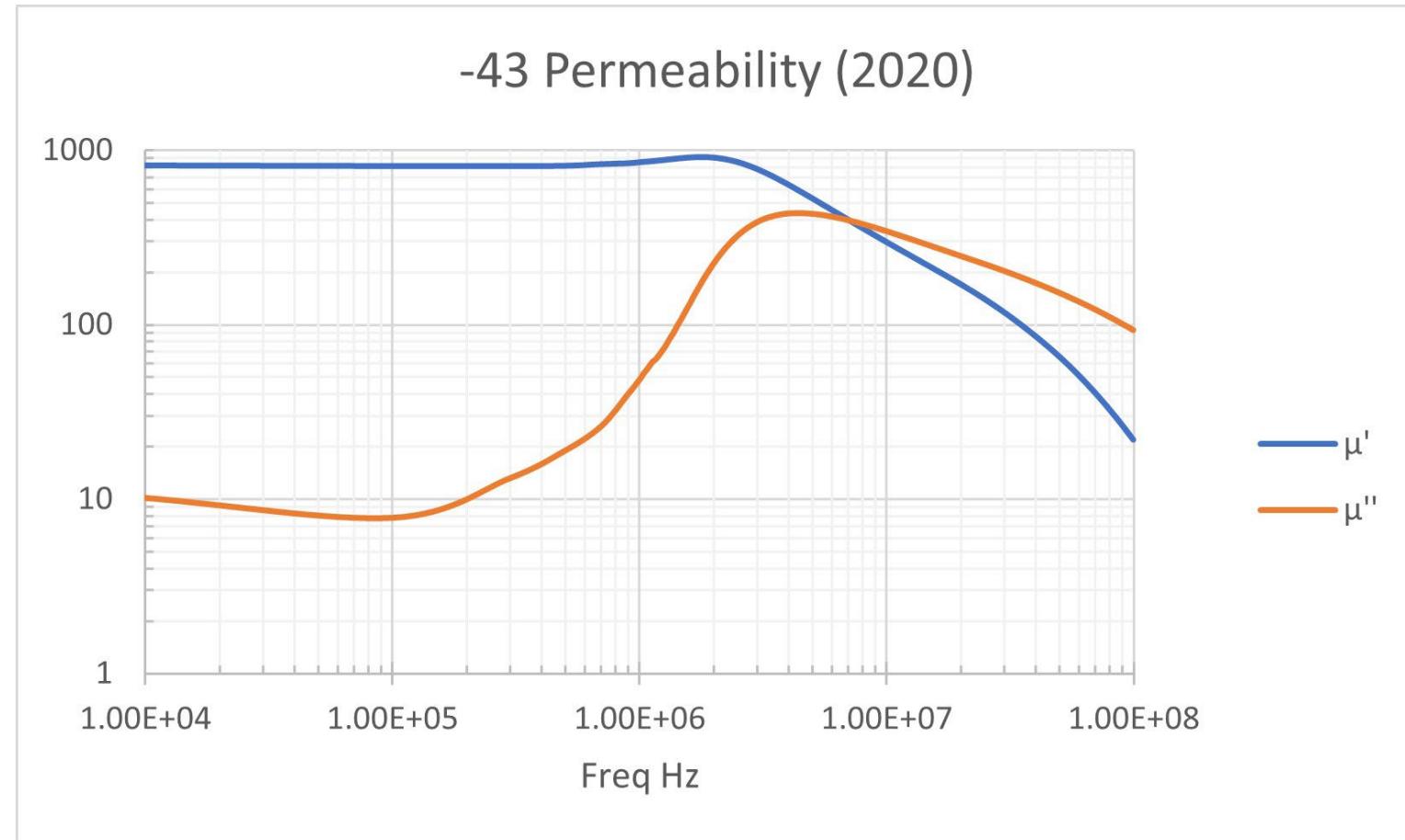- Two Elements
 - μ' Inductive
 - μ'' Resistive
- Varies with Frequency



Complex Permeability

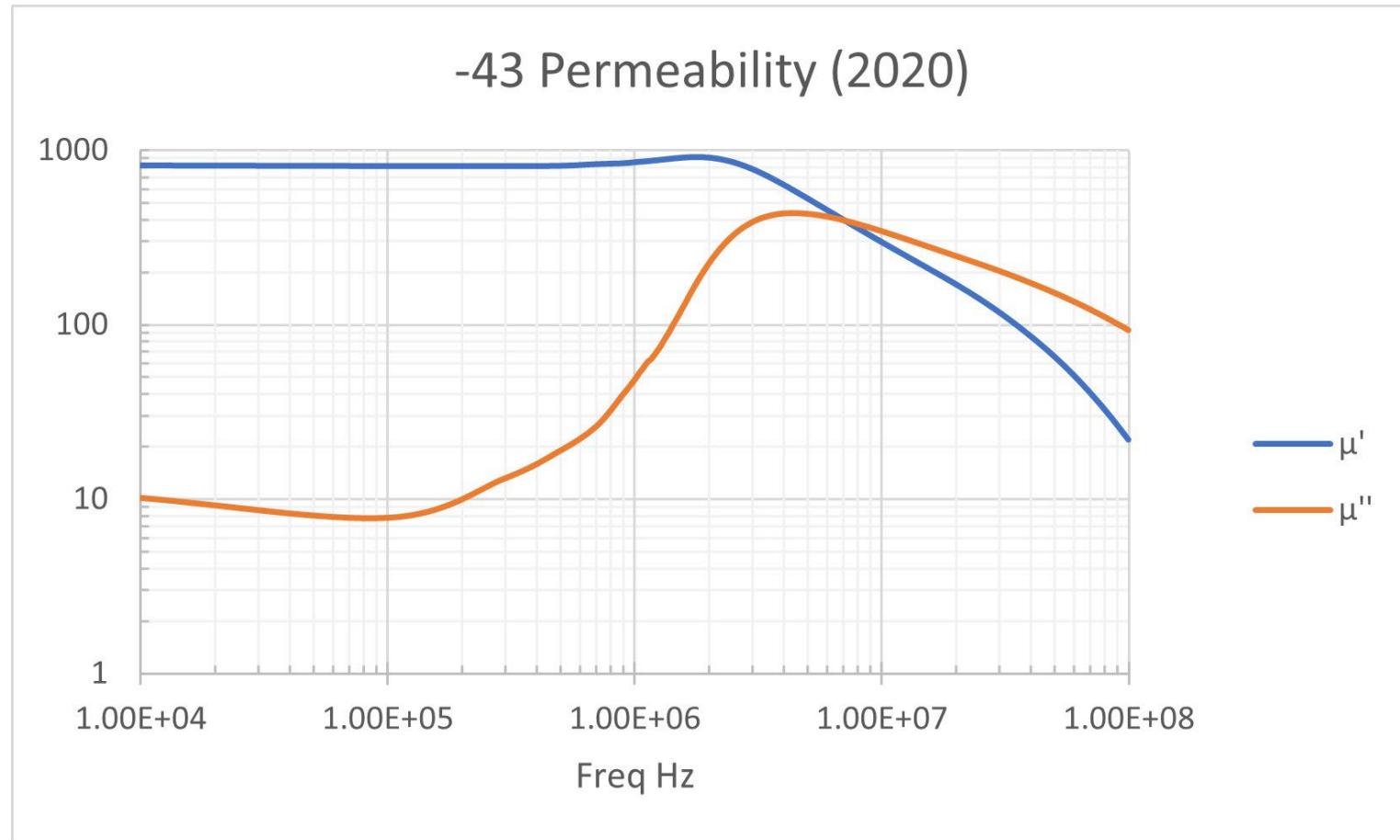- Resistive Element
 - μ''
 - Power loss – Heat!
 - Core Loss



Inductance and Impedance

- Inductance for N Turns

$$L = N^2 \frac{\mu A_{xc}}{2\pi r}$$

- A_l Specified by Manufacturer

- Depends on Core Characteristics
 - Measured at 10kHz

$$A_l = \frac{\mu A_{xc}}{2\pi r}$$

A_{xc} is cross sectional Area
r is core radius
 μ is permeability

Inductance and Impedance

- Online Inductance Calculators Use A_l

- Okay for Powered Iron Cores

$$L = N^2 A_l$$

- Not for Ferrite Cores!

- μ is Complex
 - μ Varies with Frequency
 - $\mu_i \sim 800$ for -43
 - $\mu_i \sim \mu'$ at Low Frequencies

$$A_l \left(\frac{\mu' - j\mu''}{\mu_i} \right)$$

Inductance and Impedance

- Calculate Impedance

$$Z = j2\pi fL$$

- Adjust for Complex Permeability $Z = j2\pi fN^2 A_l \left(\frac{\mu' - j\mu''}{\mu_i} \right)$

- Real and Imaginary Parts

$$Z = 2\pi fN^2 A_l \left(\frac{\mu''}{\mu_i} \right) + j2\pi fN^2 A_l \left(\frac{\mu'}{\mu_i} \right)$$

Inductance and Impedance

- Imaginary is Reactance
- Real is Resistive
 - Dissipates Power
 - Core Loss

$$X = 2\pi f N^2 A_l \left(\frac{\mu'}{\mu_i} \right)$$


$$L = N^2 A_l \left(\frac{\mu'}{\mu_i} \right)$$

$$R = 2\pi f N^2 A_l \left(\frac{\mu''}{\mu_i} \right)$$

Inductance vs. Frequency

$$L = N^2 A_l \left(\frac{\mu'}{\mu_i} \right)$$

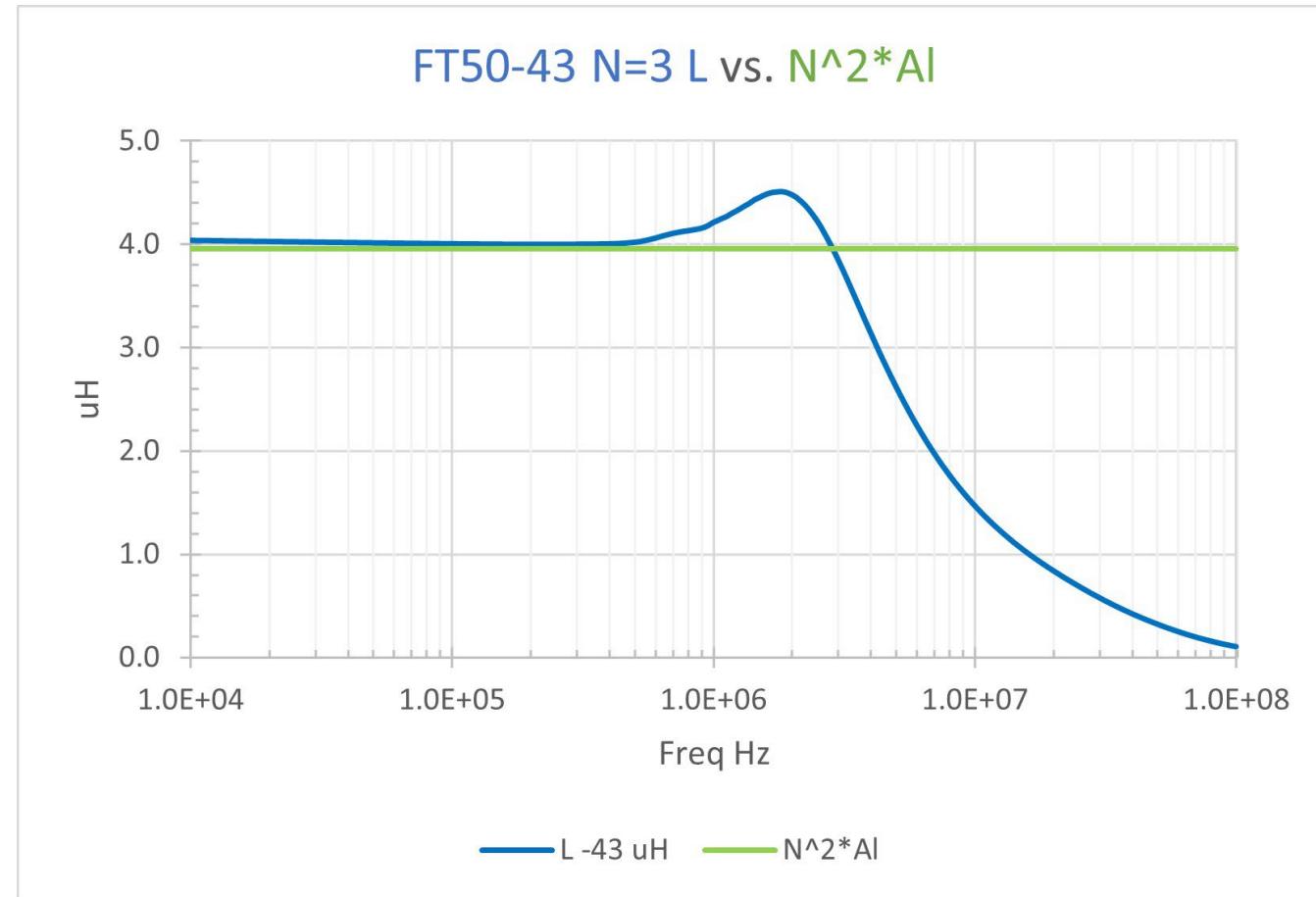
- A_l Specified by Manufacturer
- $A_l \sim 440$ FT50-43
- $\mu_i \sim \mu'$ at Low Frequencies



Resistance vs. Frequency


$$R = 2\pi f N^2 A_l \left(\frac{\mu''}{\mu_i} \right)$$

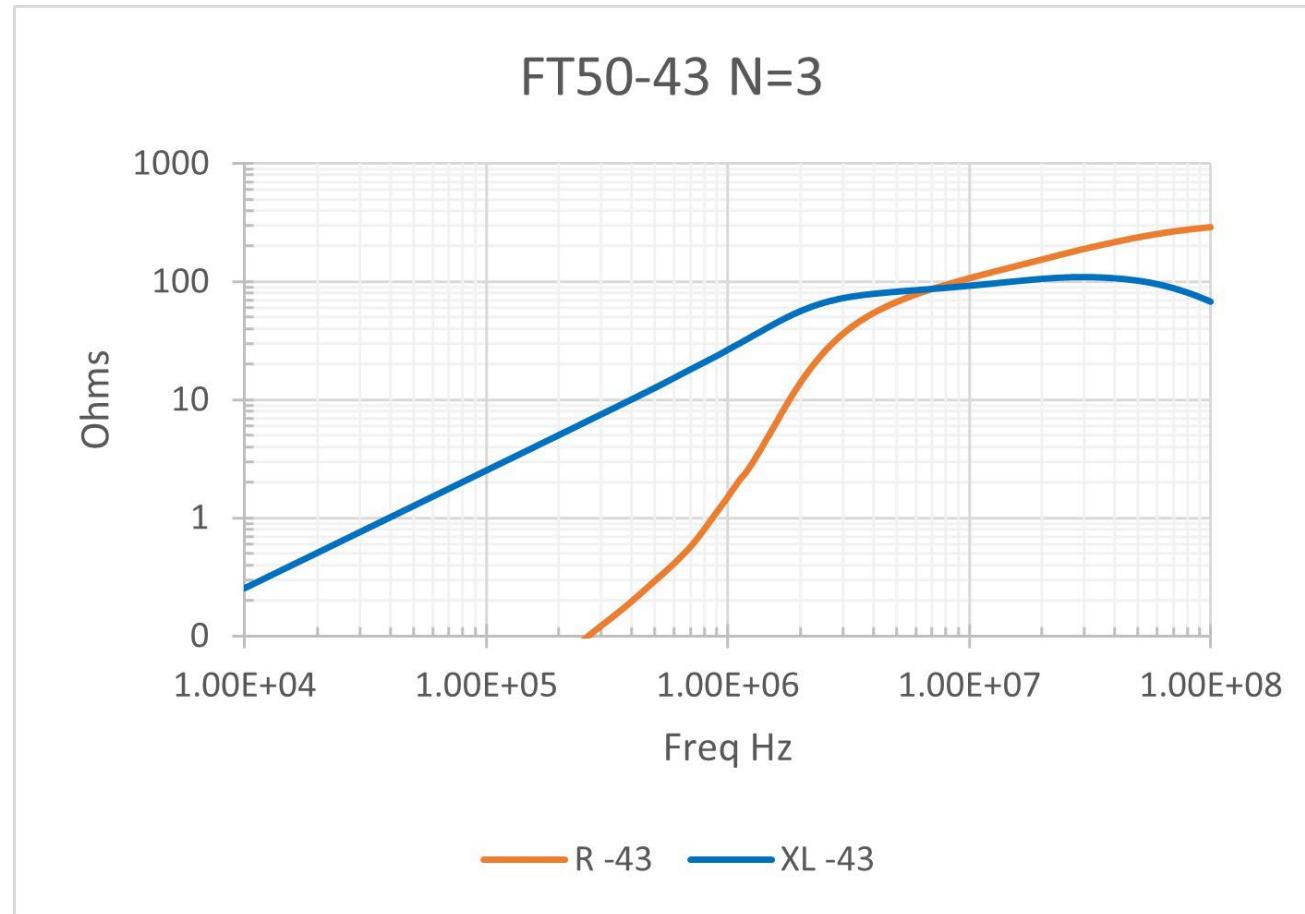- Becomes Significant at High Frequencies




Measuring Transformer Loss

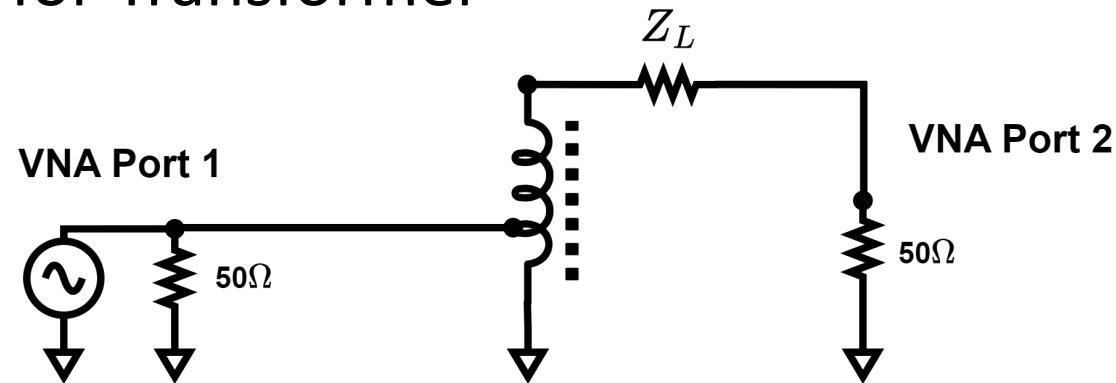
- First Method
- Single Transformer with Resistor Load
 - Resistor plus 50Ω Port 2 Impedance
 - ‘Antenna’ Load for Transformer



Tapped Transformer

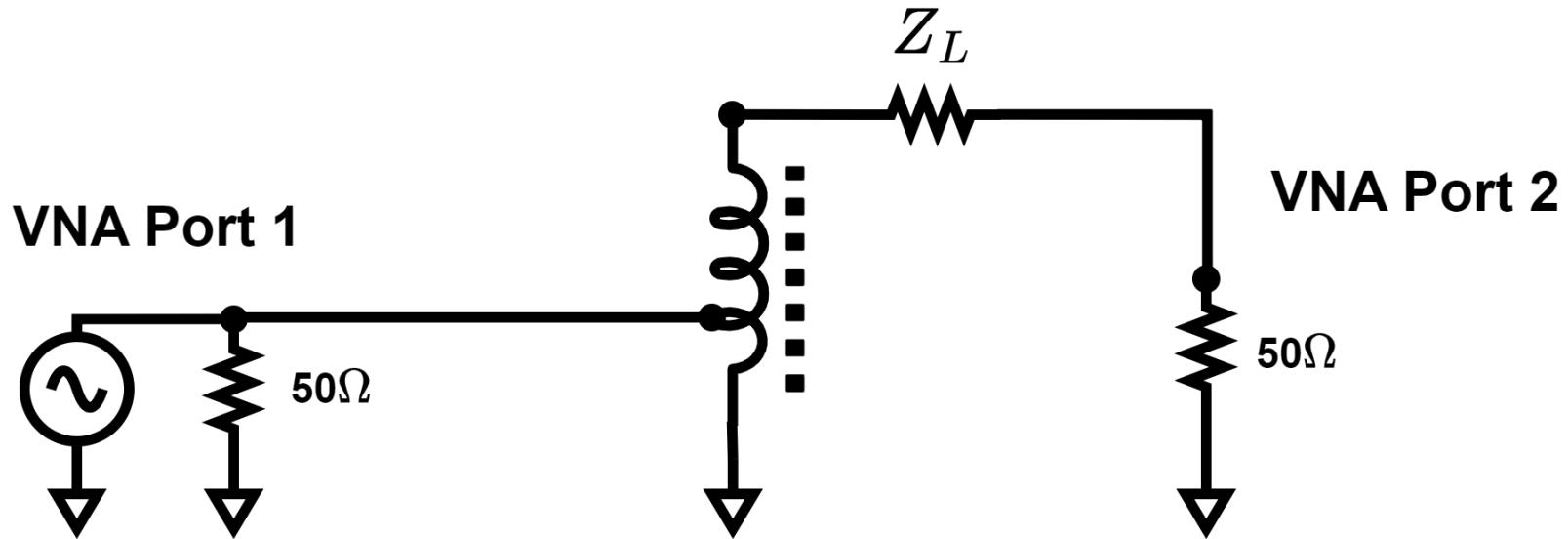

Linked Transformer

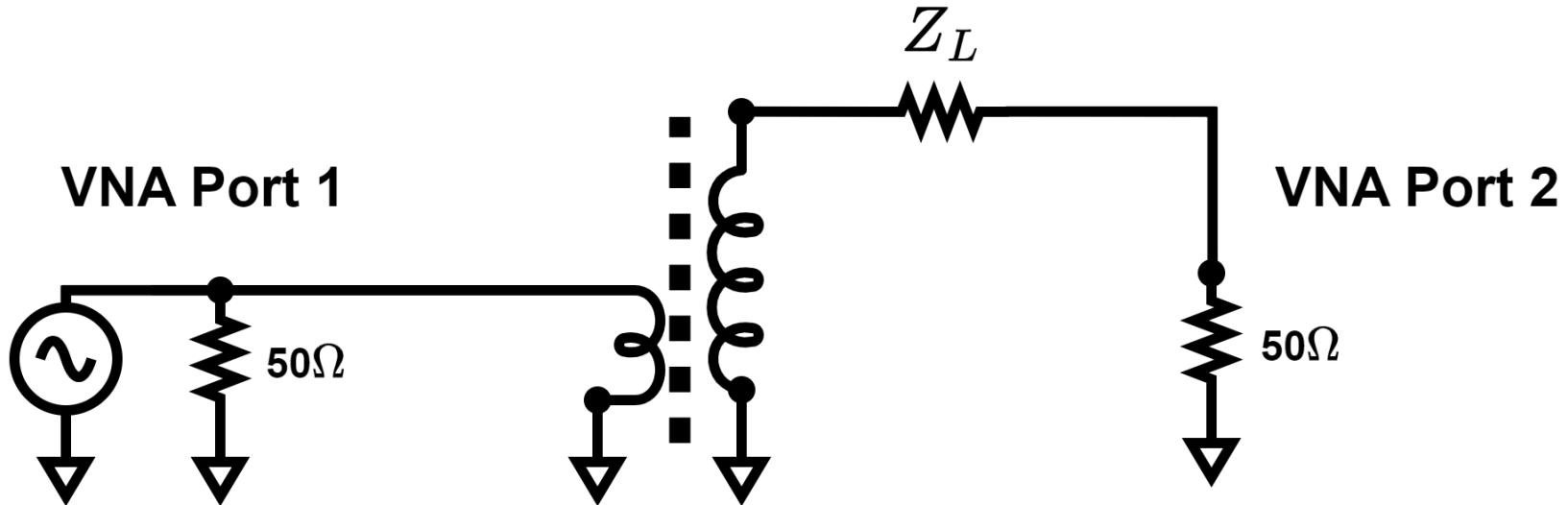

Measurement Parameters


- VNA Measures ‘Insertion Loss’

- $S_{21} = V(\text{port2})/V(\text{port1})$

- Load Resistor Z_L


- 2400Ω for 1:49

- 4000Ω for 1:81

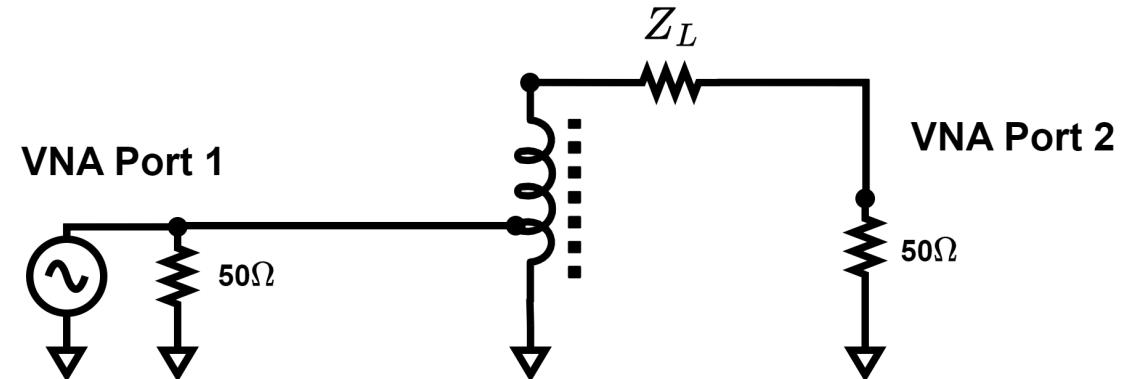


Measurement Parameters

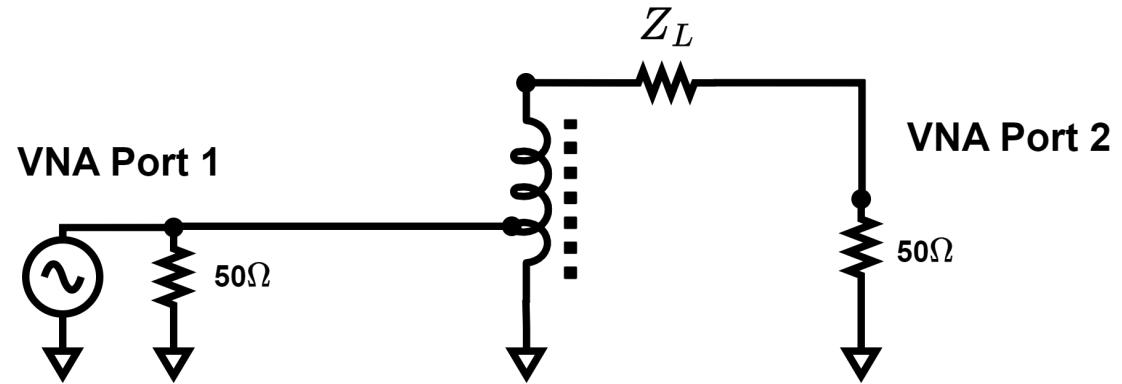
- Transformer Loss
 - Power Loss in dB
 - Efficiency Equivalent
 - $\text{eff}(\%) = 100 \times 10^{-(\text{xfmr}_{loss}(dB)/10)}$



Insertion Loss

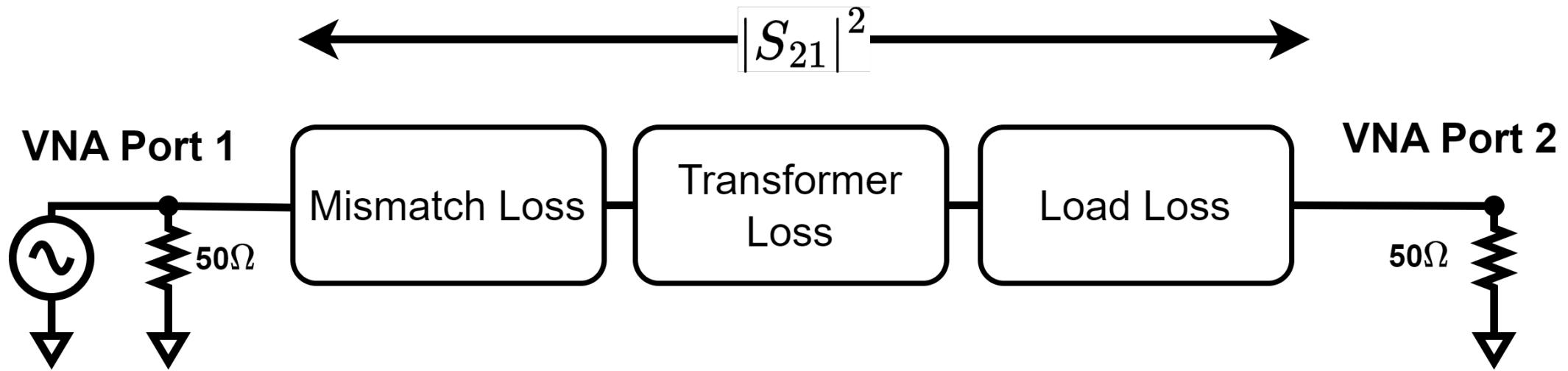


Mismatch Loss

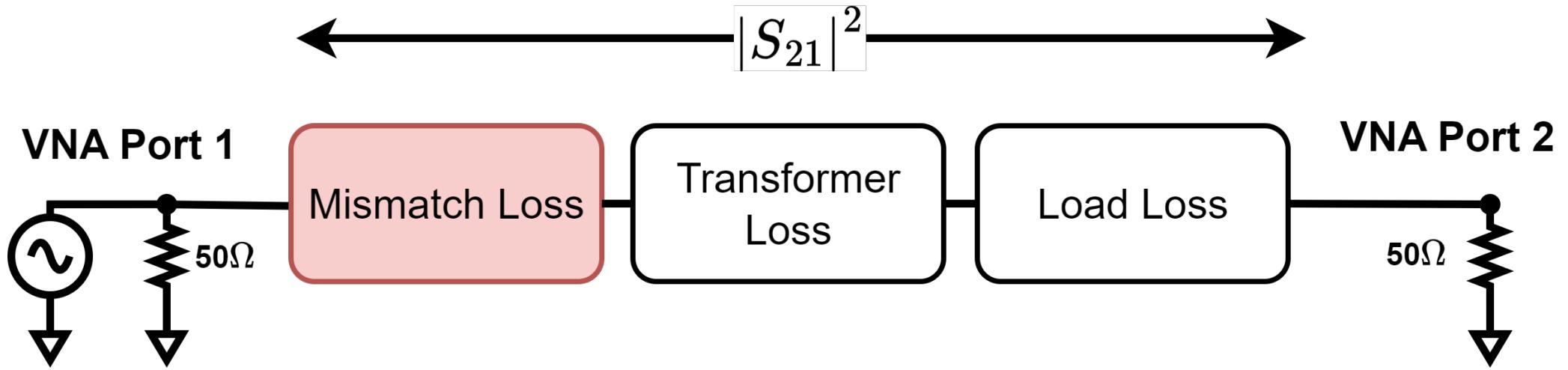

$$MM_{loss}(dB) = -10 \log\left(1 - |S_{11}|^2\right)$$


Load Loss

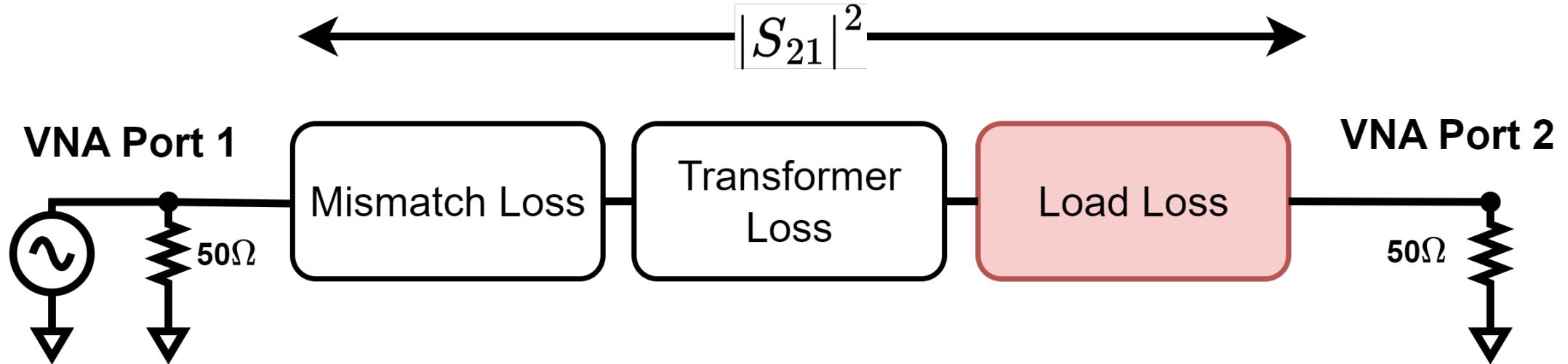

- Series Measurement of Z_L as a Complex Impedance
 - Separate Measurement – Don't Assume a Pure Resistance

$$Load_{loss}(dB) = 10 \log \left(|S_{21}(Z_L)|^2 / \left(1 - |S_{11}(Z_L)|^2 \right) \right)$$

Transformer Loss

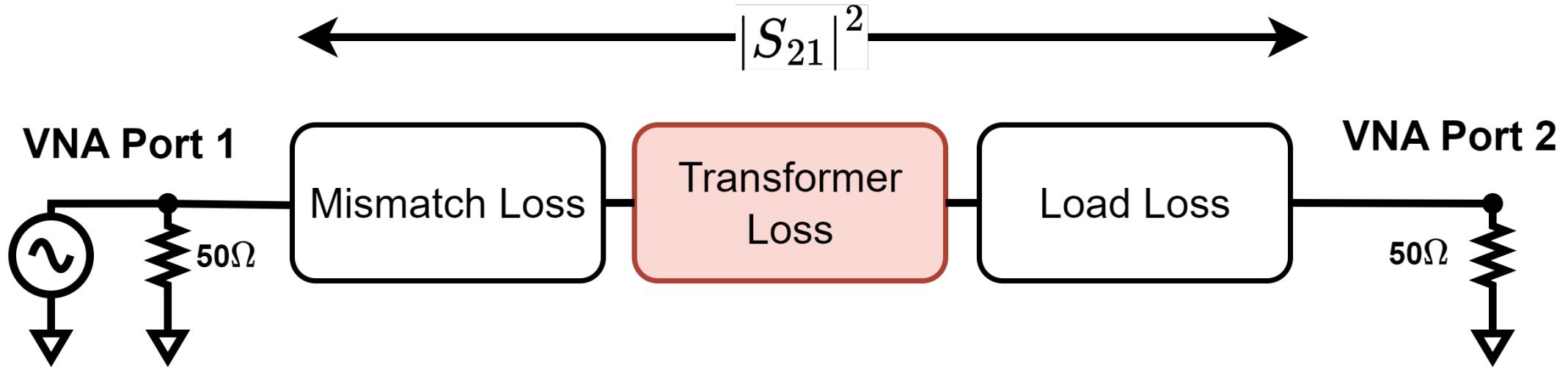

- Transformer Loss

$$\text{xfmr}_{loss}(dB) = 10 \log(|S_{21}|^2) - MM_{loss}(dB) - Load_{loss}(dB)$$



Measuring Transformer Loss

- Use nanoVNA With a Test Fixture
 - Recommend Idle for > 15 minutes
 - Calibrate nanoVNA and Test Fixture
 - Open, Short, Load, Isolate, Through
 - Over Test Frequency Range


Measuring Transformer Loss

- Use Test Fixture
 - Better Repeatability
 - Connect Directly to NanoVNA
 - Part of Test Calibration
 - Direct Ground Connection Between Ports
 - Headers for Configuration Change


Test Fixture

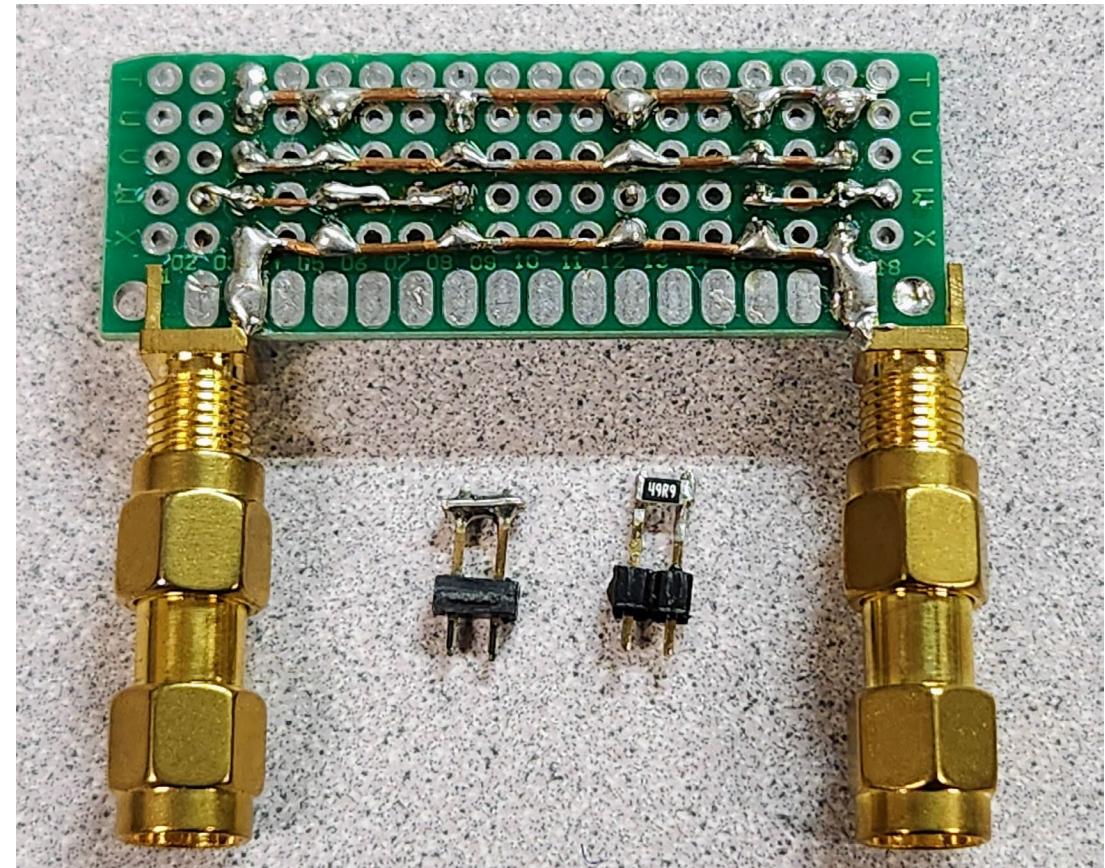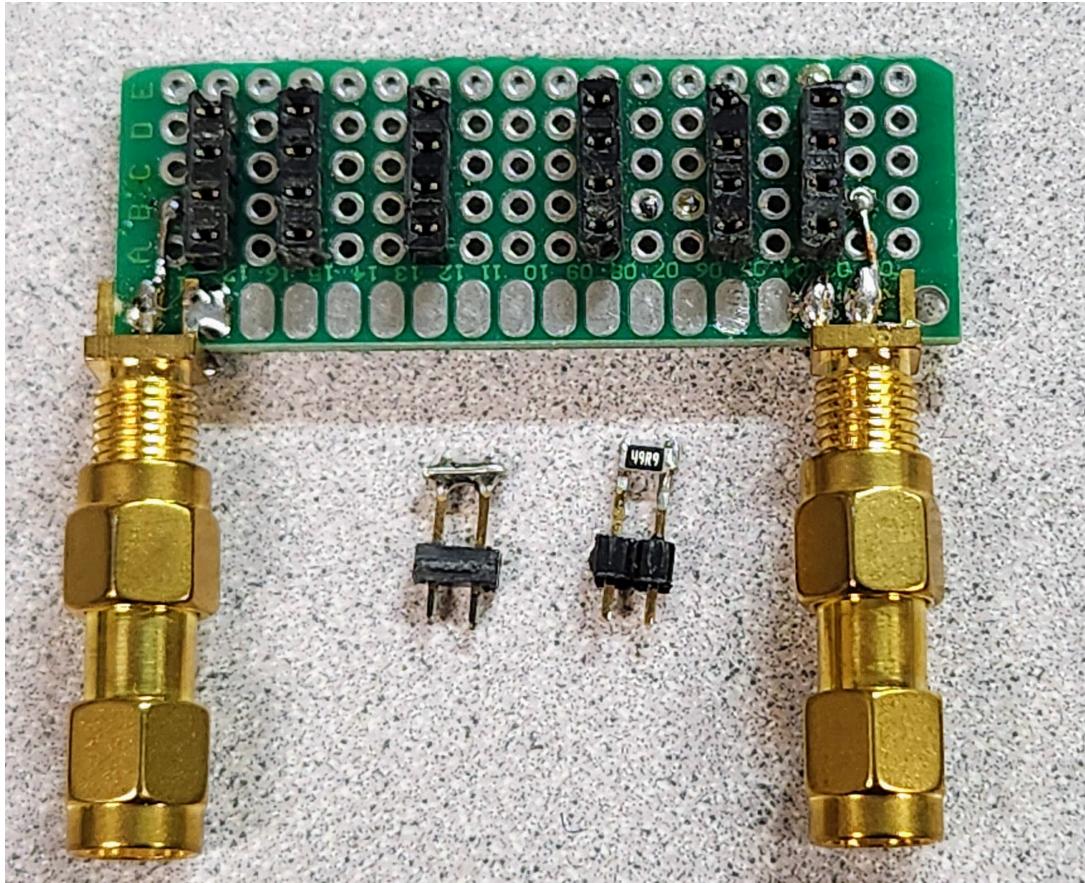

Test Fixture

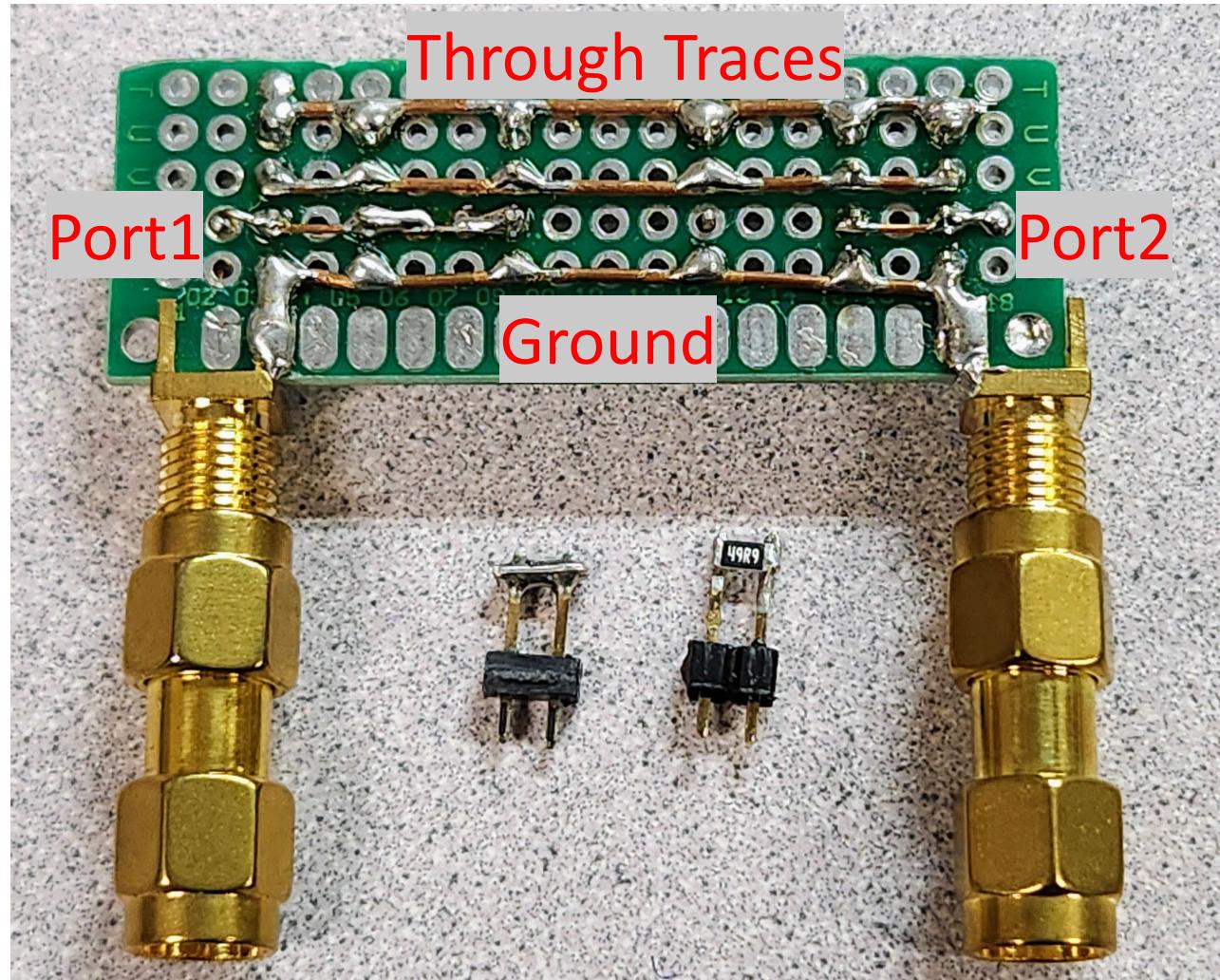


50 Ohm Load Port1 Calibration

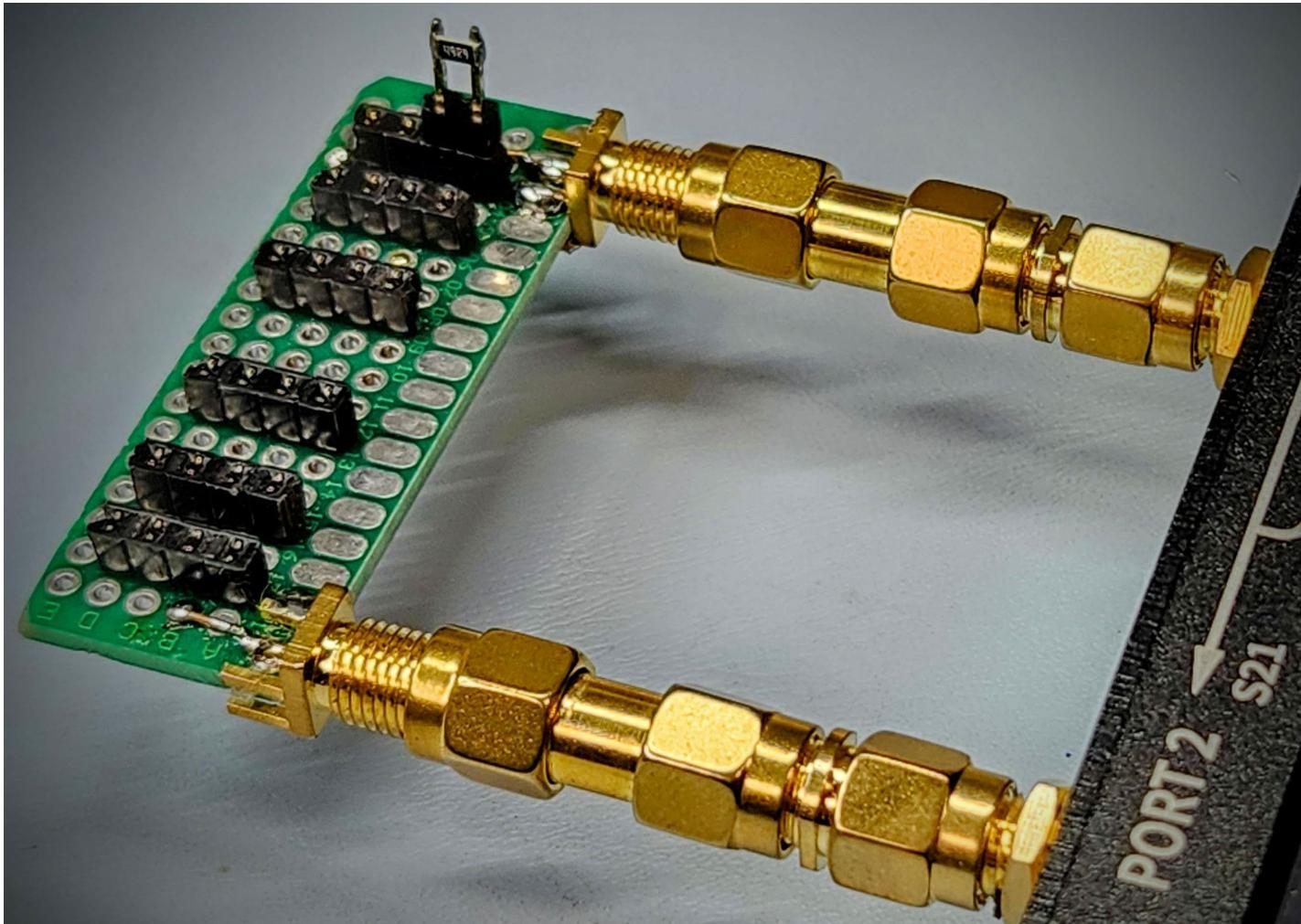

Measuring Transformer Loss


- Measure Load Resistor In Test Fixture
 - Over Test Frequency Range
 - Series Through Measurement
 - Load S2P (F S11 S21 R I) Data into Spread Sheet
 - <https://github.com/phase2682/FC-XFMRS-AI6XG>

Load Resistor Characterization

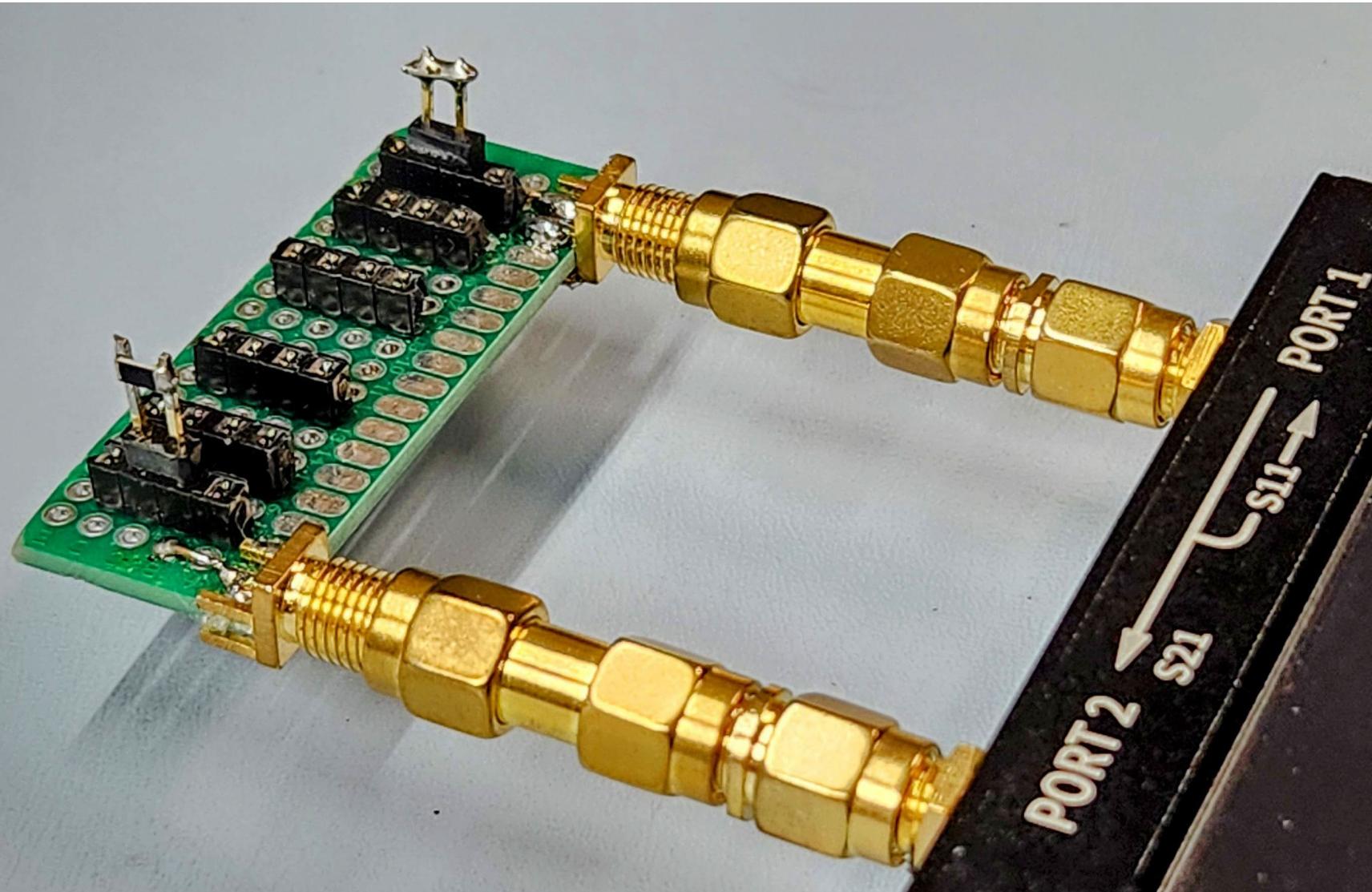


Measuring Transformer Loss

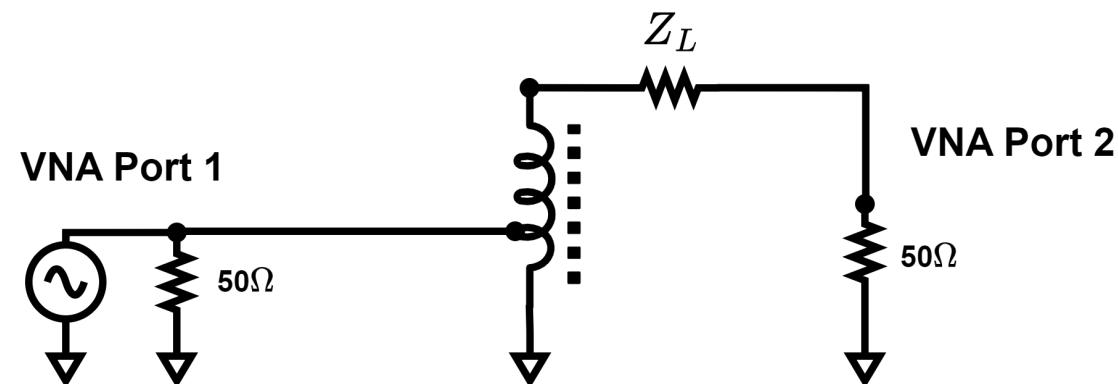
- Put Transformer and Load Resistor in Test Fixture
 - Test Circuit Configuration
 - Load S2P (F S11 S21 R I) Data into Spread Sheet
 - Calculate Transformer Loss




Measuring Transformer Loss

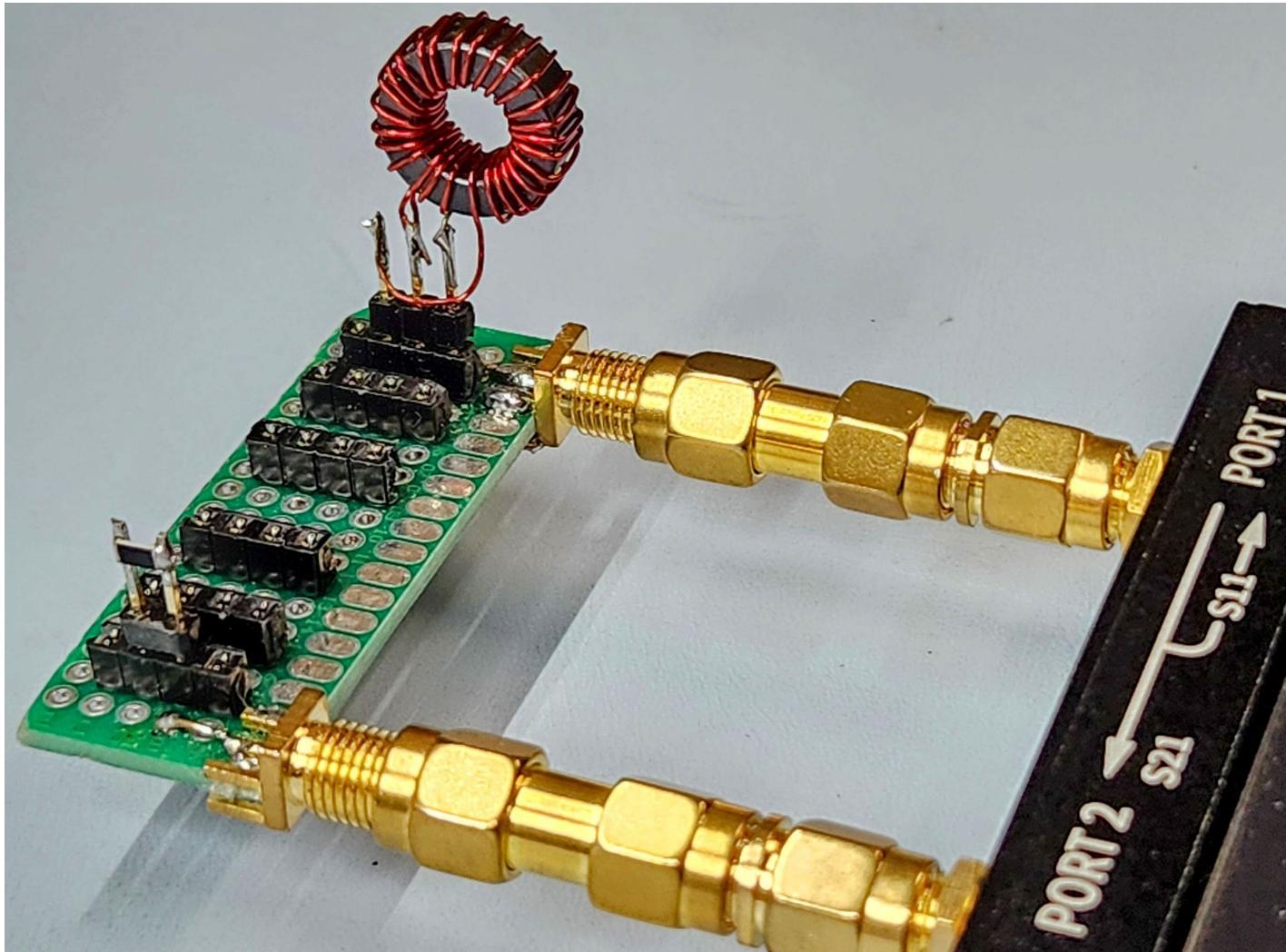



FT50-43 3:27 SOTA Transformer

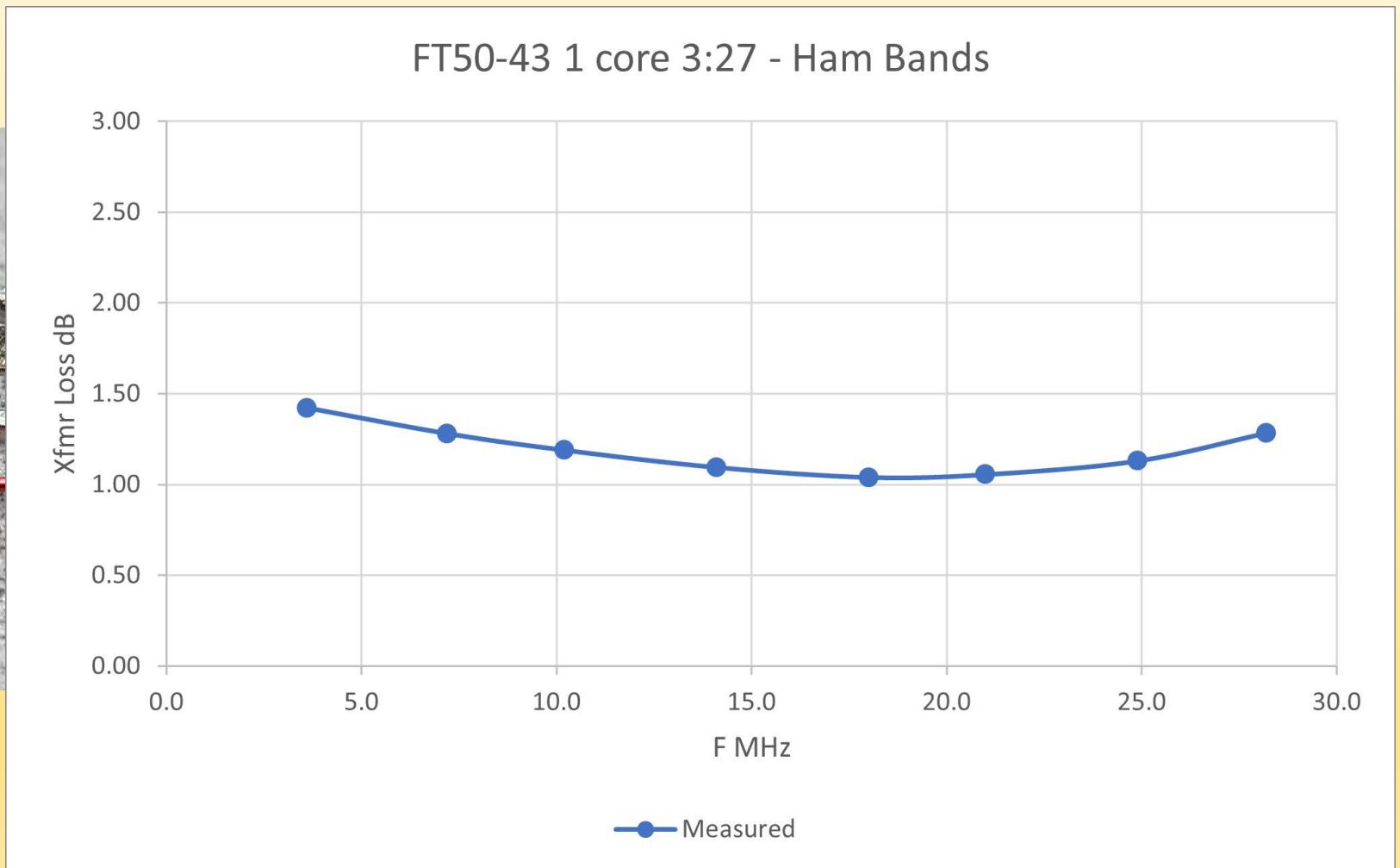

2643625002 2:18 SOTA Transformer

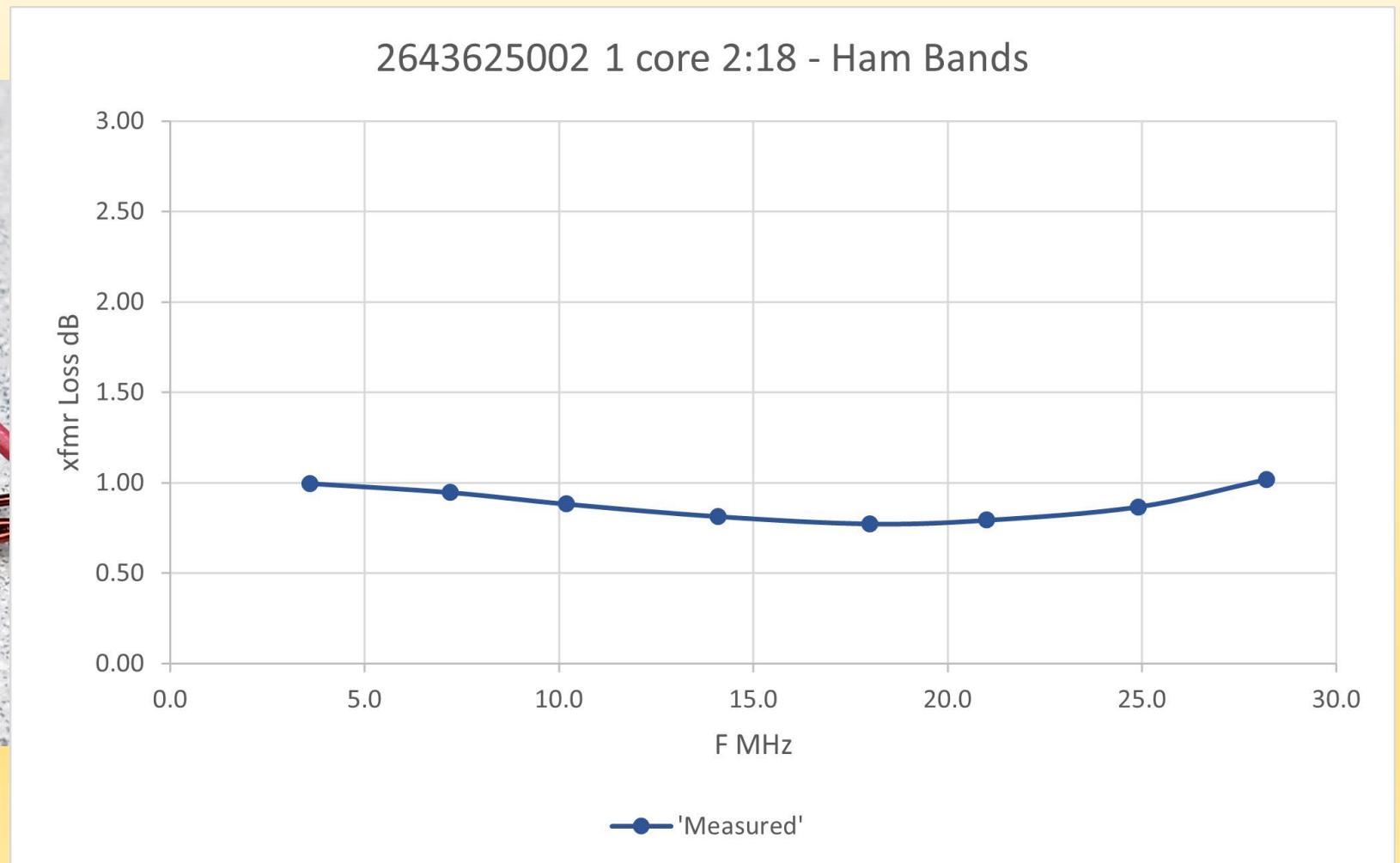


FT240-43 2:14 2 Cores QRO Transformer

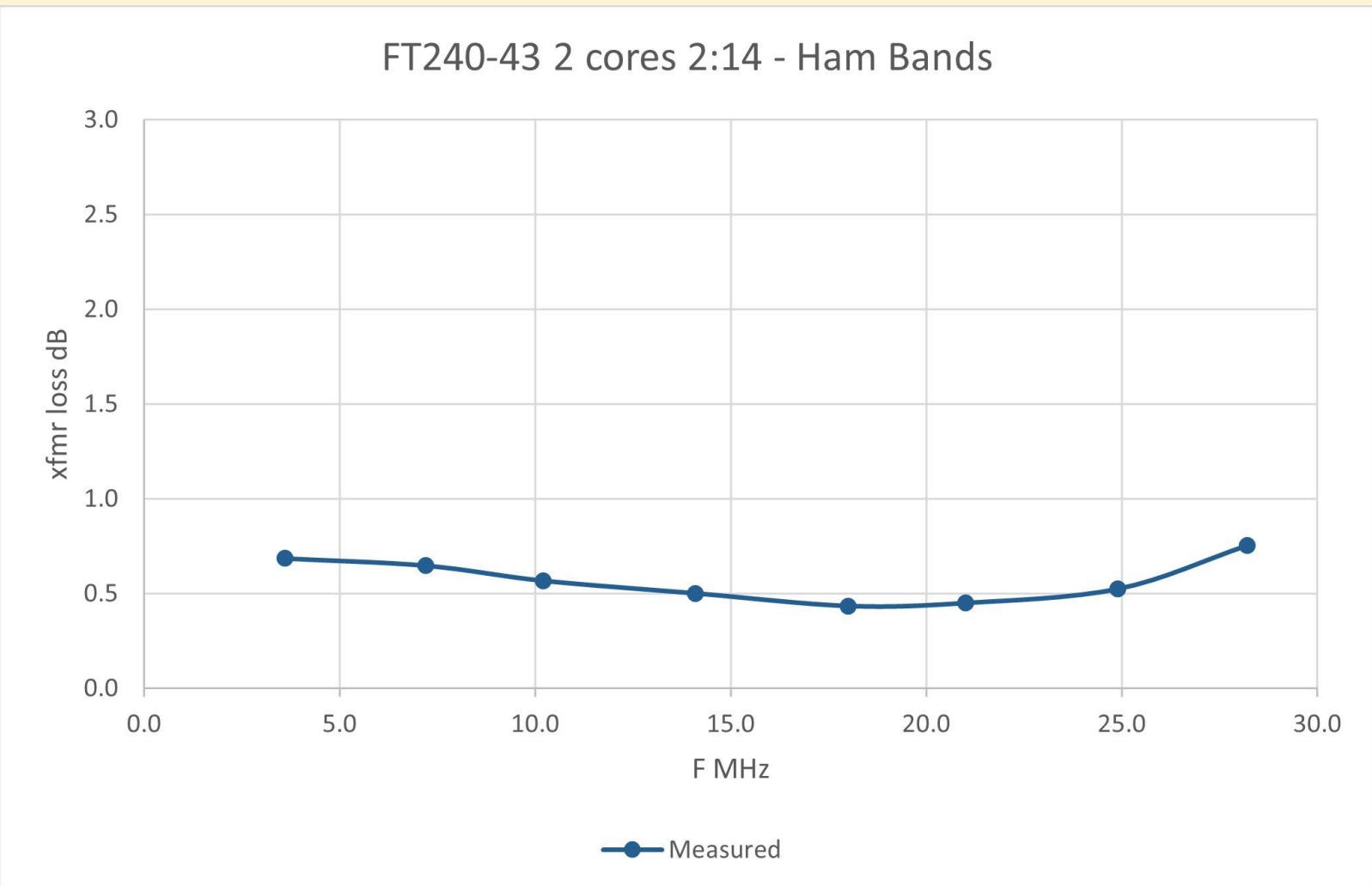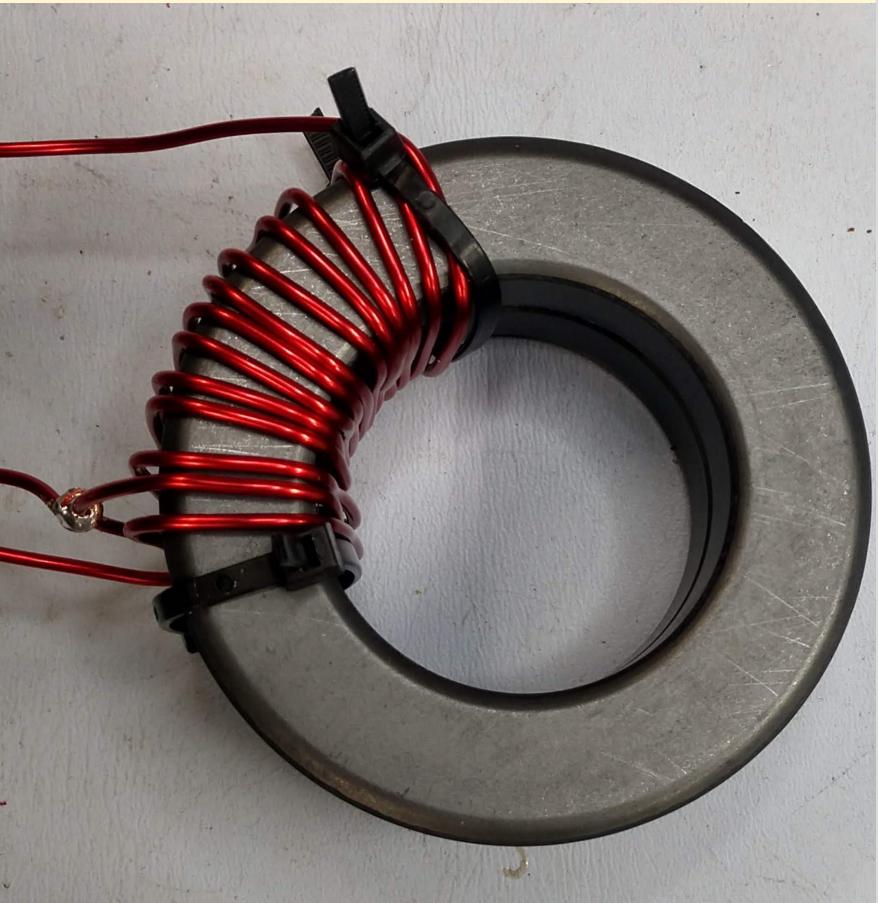


Estimate Transformer Loss

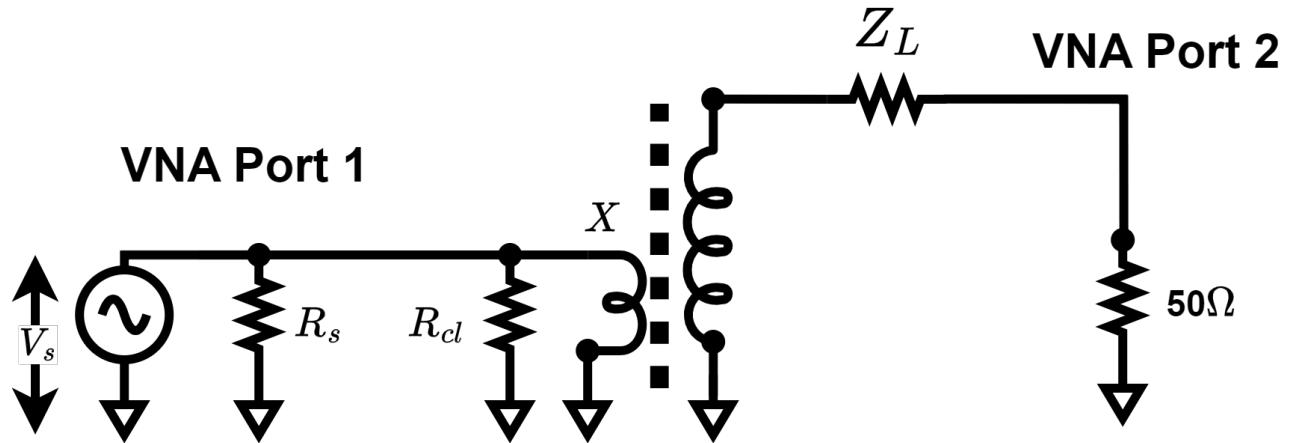- Core Loss as an Estimate
 - X and R in Transformer
- Source Power
 - V_s^2 / R_s
- Power Loss in R_{cl}
 - V_s^2 / R_{cl}



Estimate Transformer Loss

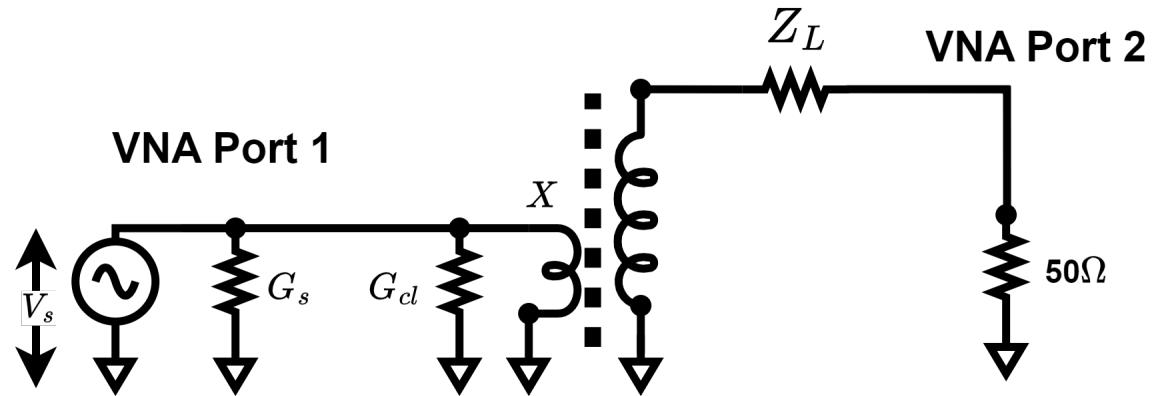- Use Conductance
 - $V_s^2 G_s \quad V_s^2 G_{cl}$
- Power Out of Transformer
 - $V_s^2 G_s - V_s^2 G_{cl}$
- Efficiency
 - $(V_s^2 G_s - V_s^2 G_{cl}) / (V_s^2 G_s) = 1 - G_{cl}/G_s$
 - $\text{Core}_{loss}(dB) = -10 \log(1 - G_{cl}/G_s)$



Estimate Transformer Loss

- To Determine Conductance for Transformer
 - Calculate Z First
 - $Z = 2\pi f N^2 A_l \left(\frac{\mu''}{\mu_i} \right) + j 2\pi f N^2 A_l \left(\frac{\mu'}{\mu_i} \right)$
 - Then Calculate $1/Z = Y$ as a Complex Number
 - $1/(a + jb) = (a - jb)/(a^2 + b^2)$
 - Y is Admittance
 - Conductance is Real Portion of Y
 - N is Primary Turns

Estimate Transformer Loss

- Excel Spread Sheet Available
 - FT50-43, FT240-43, 2643625002
- Permeability, Dimensions
- Input Freq, N turns, # of cores
- Calculates:
 - Z, Y, L
 - Efficiency %,
 - Loss(dB)

Calculator for Fair-rite FT50-43 series Physical dimensions from toroids.info		
number of cores	1	
Frequency (MHz)	7.2	
Outer Dia. (mm)	12.7	toroids.info
Inner Dia. (mm)	7.15	toroids.info
width/height (mm)	4.9	toroids.info
μ^t	394.5	auto fill for
μ^u	394.6	HF ham bands
Turns	3	
Cs (pFd)	0	
AI (nH)	222.10	
$\Sigma A/I$ (m) flux crowding	0.0004480	
real	imaginary	
Y (S)	0.005529	-0.005528
Z (Ω)	90.5	90.4
$ Z $ (Ω)	127.9	
Ls (μH)	1.999	
winding length (cm)(inch)	10.6	4.2
winding length (cm)(inch)	12.8	5.0
expected efficiency	72.4%	
expected loss dB	1.405	

Compare With Online Calculator

Inputs:	
Frequency (MHz)	7.200
A _L (nH)	440.0
μ_i	800.0
μ'	394.5
μ''	394.6
Turns	3.0
C _s (pF)	0.000
<input type="button" value="Calculate"/>	
Results:	
$\Sigma A/I$ (m)	0.0004377
Y (S)	0.00566-j0.00566
Z (Ω)	88.4+j88.3
Z (Ω)	125
L _s (μ H)	1.95

<https://owenduffy.net/calc/toroid2.htm> Using A_L and μ_i

		Calculator for Fair-rite FT50-43 series Physical dimensions from toroids.info	
number of cores	1		
Frequency (MHz)	7.2		
Outer Dia. (mm)	12.7	toroids.info	
Inner Dia. (mm)	7.15	toroids.info	
width/height (mm)	4.9	toroids.info	
μ'	394.5	auto fill for	
μ''	394.6	HF ham bands	
Turns	3		
C _s (pFd)	0		
<input type="button" value="Σ"/>		<input type="button" value="Σ"/>	
A _L (nH)	222.10	cii	
$\Sigma A/I$ (m) flux crowding	0.0004480	Sr	
real	imaginary	Sr	
Y (S)	0.005529	-0.005528	
Z (Ω)	90.5	90.4	
Z (Ω)	127.9		
L _s (μ H)	1.999		
winding length (cm)(inch)	10.6	4.2	
winding length (cm)(inch)	12.8	5.0	
expected effeciency	72.4%		
expected loss dB	1.405		


Compare With Online Calculator

Inputs:	
Frequency (MHz)	7.20
OD (mm)	12.70
ID (mm)	7.150
Width (mm)	4.900
Chamfer (mm)	0
μ'	394.5
μ''	394.6
Turns	3.0
Cs (pF)	0.000
<input type="button" value="Calculate"/>	
Results:	
$\Sigma A/l$ (m)	0.0004480
Y (S)	0.00553-j0.00553
Z (Ω)	90.5+j90.4
Z (Ω)	128
Ls (μH)	2.00


<https://owenduffy.net/calc/toroid.htm> Using Rectangular Cross-section Estimate

		Calculator for Fair-rite FT50-43 series Physical dimensions from toroids.info	
number of cores	1		
Frequency (MHz)	7.2		
Outer Dia. (mm)	12.7	toroids.info	
Inner Dia. (mm)	7.15	toroids.info	
width/height (mm)	4.9	toroids.info	
μ'	394.5	auto fill for	
μ''	394.6	HF ham bands	
Turns	3		
Cs (pFd)	0		
AI (nH)	222.10		
$\Sigma A/l$ (m) flux crowding	0.0004480		
real	imaginary		
Y (S)	0.005529	-0.005528	
Z (Ω)	90.5	90.4	
Z (Ω)	127.9		
Ls (μH)	1.999		
winding length (cm)(inch)	10.6	4.2	
winding length (cm)(inch)	12.8	5.0	
expected effeciency	72.4%		
expected loss dB	1.405		


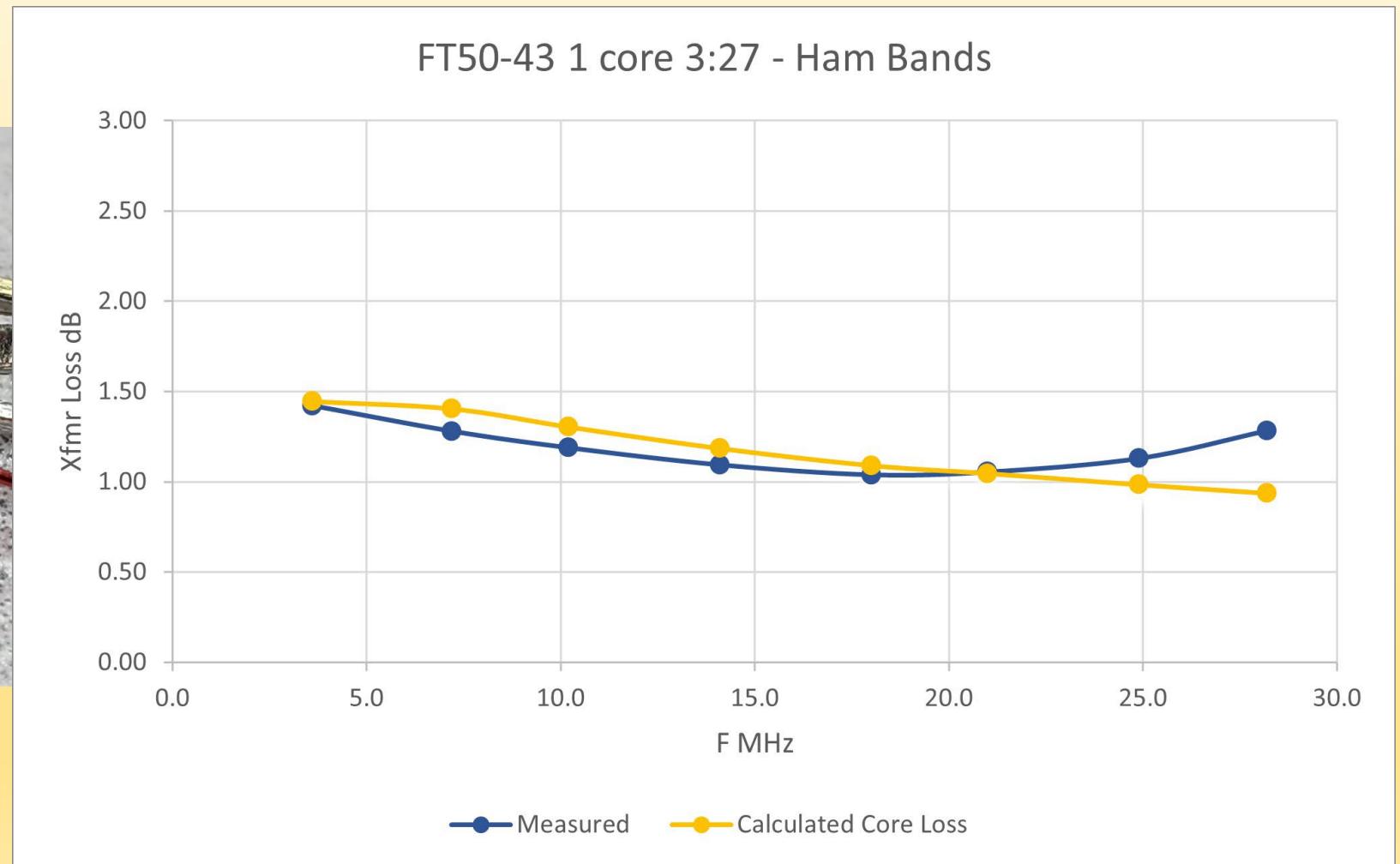
FT50-43 3:27 SOTA Transformer vs. Core Loss



2643625002 2:18 SOTA Transformer

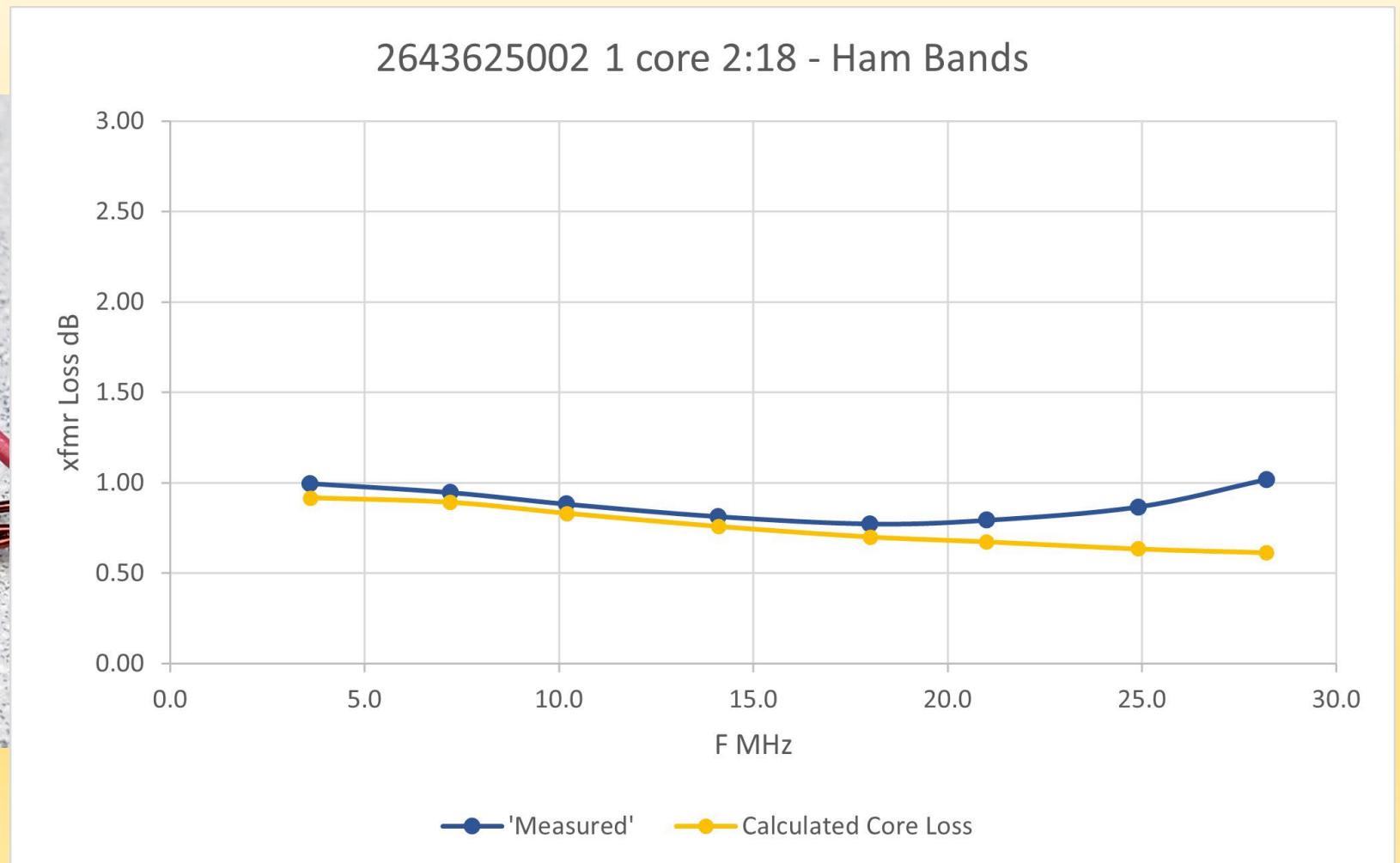

FT240-43 2:14 2 Cores QRO Transformer

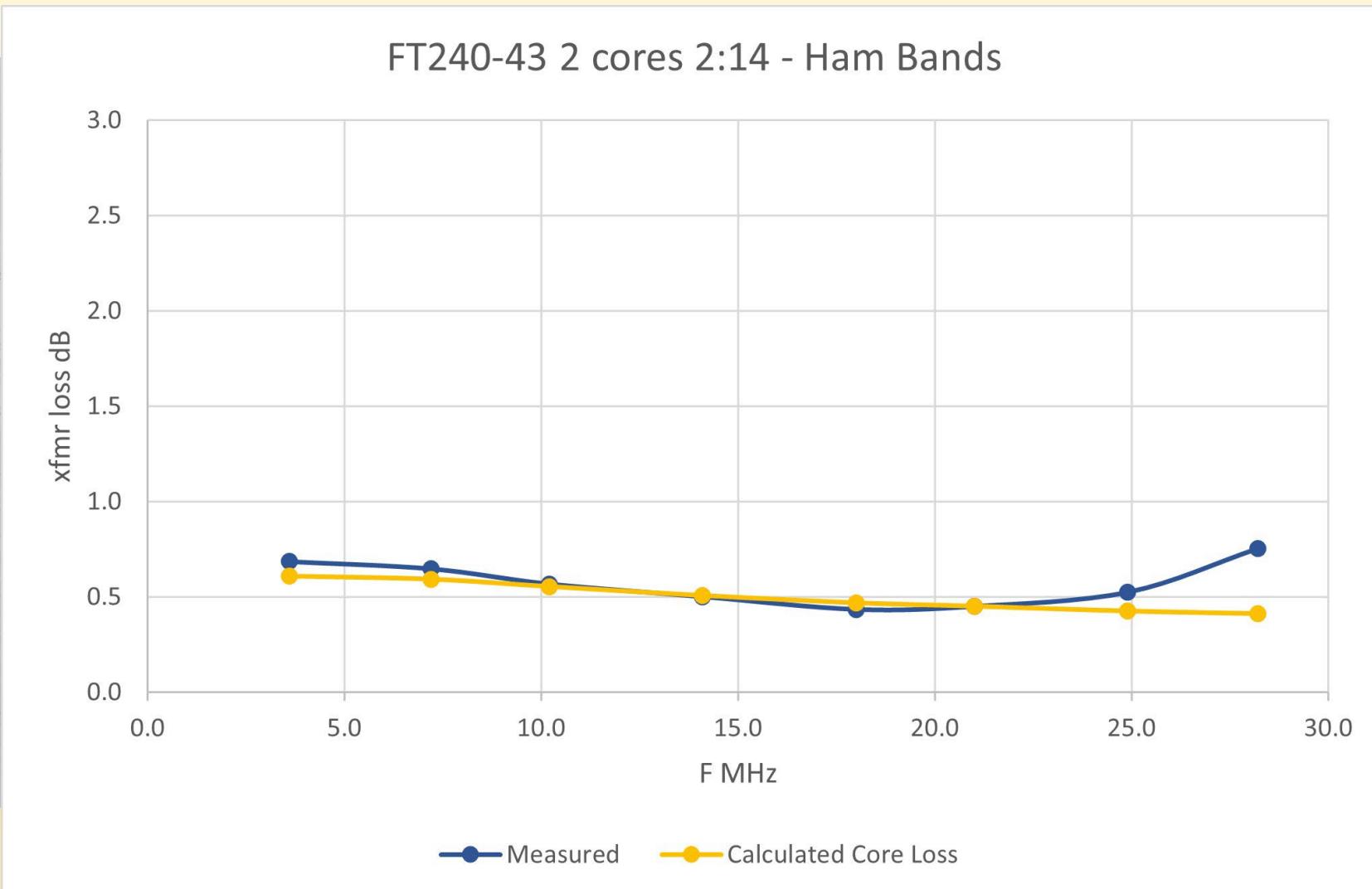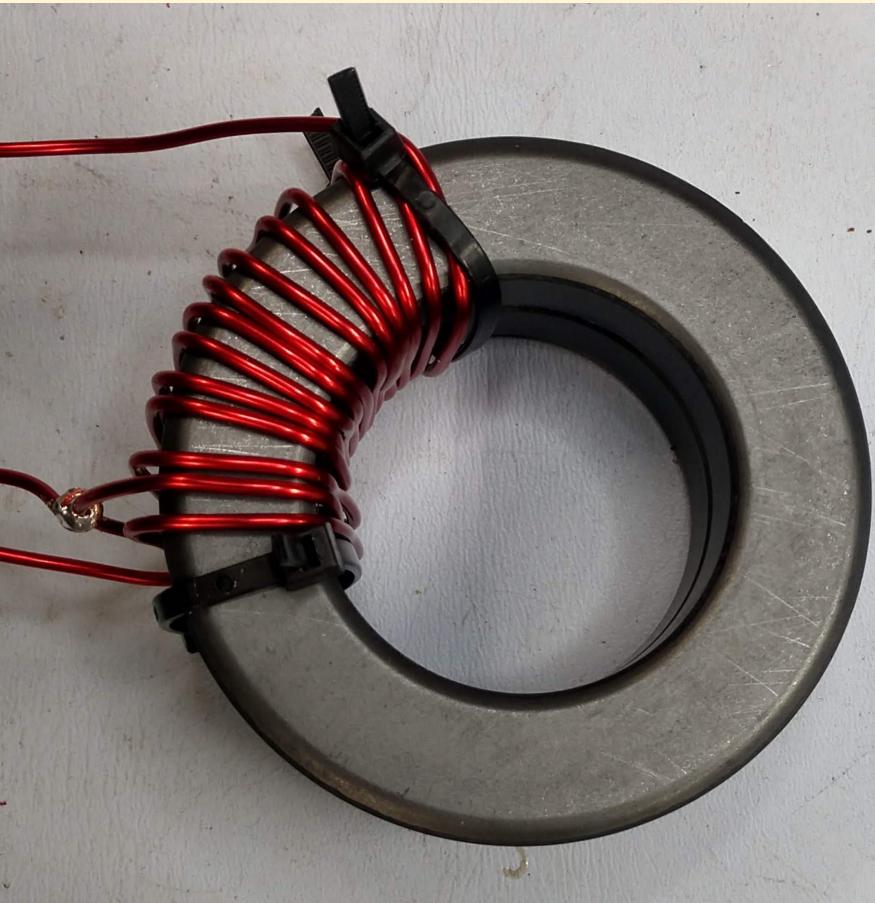


Measured vs. Core Loss

- Core Loss Dominant for Low HF Bands
- Other Losses at Higher Frequencies
 - Leakage Inductance
 - Winding Capacitance
- Core Loss Can be a Good Estimate of Transformer Loss for HF Bands


Measuring Transformer Loss

- Second Method
- Two Transformers
 - Back-to-Back
 - No Resistor Load
 - $|S_{21}|$ Insertion Loss
 - Wind Two Identical Transformers
- Often Used to Show Effect of Primary Capacitors


Back-to-Back Transformers

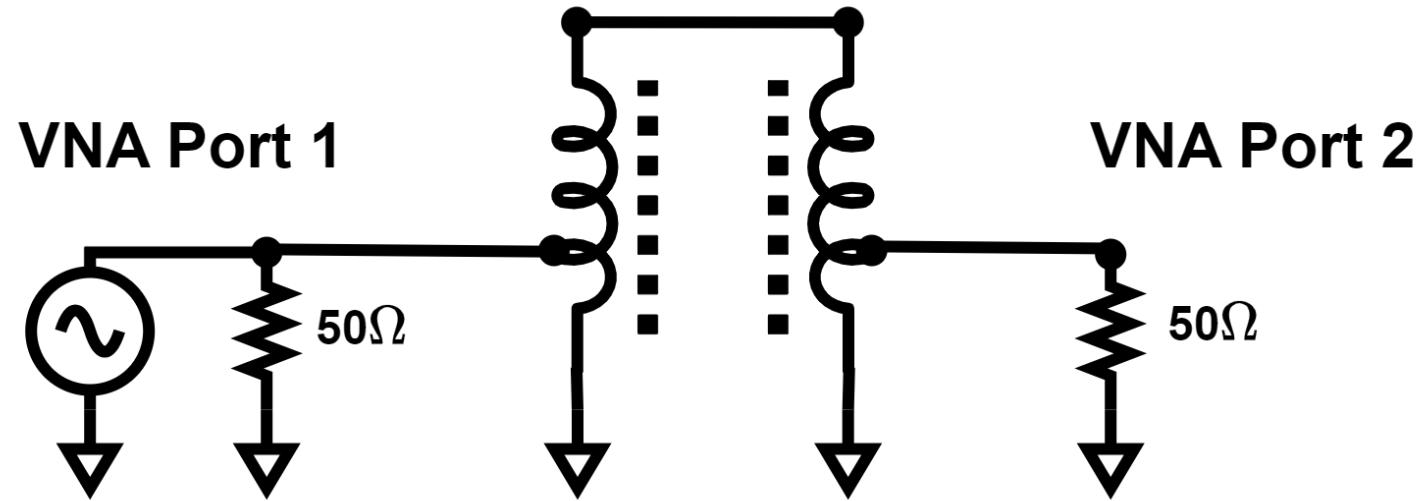


Back-to-Back Transformers

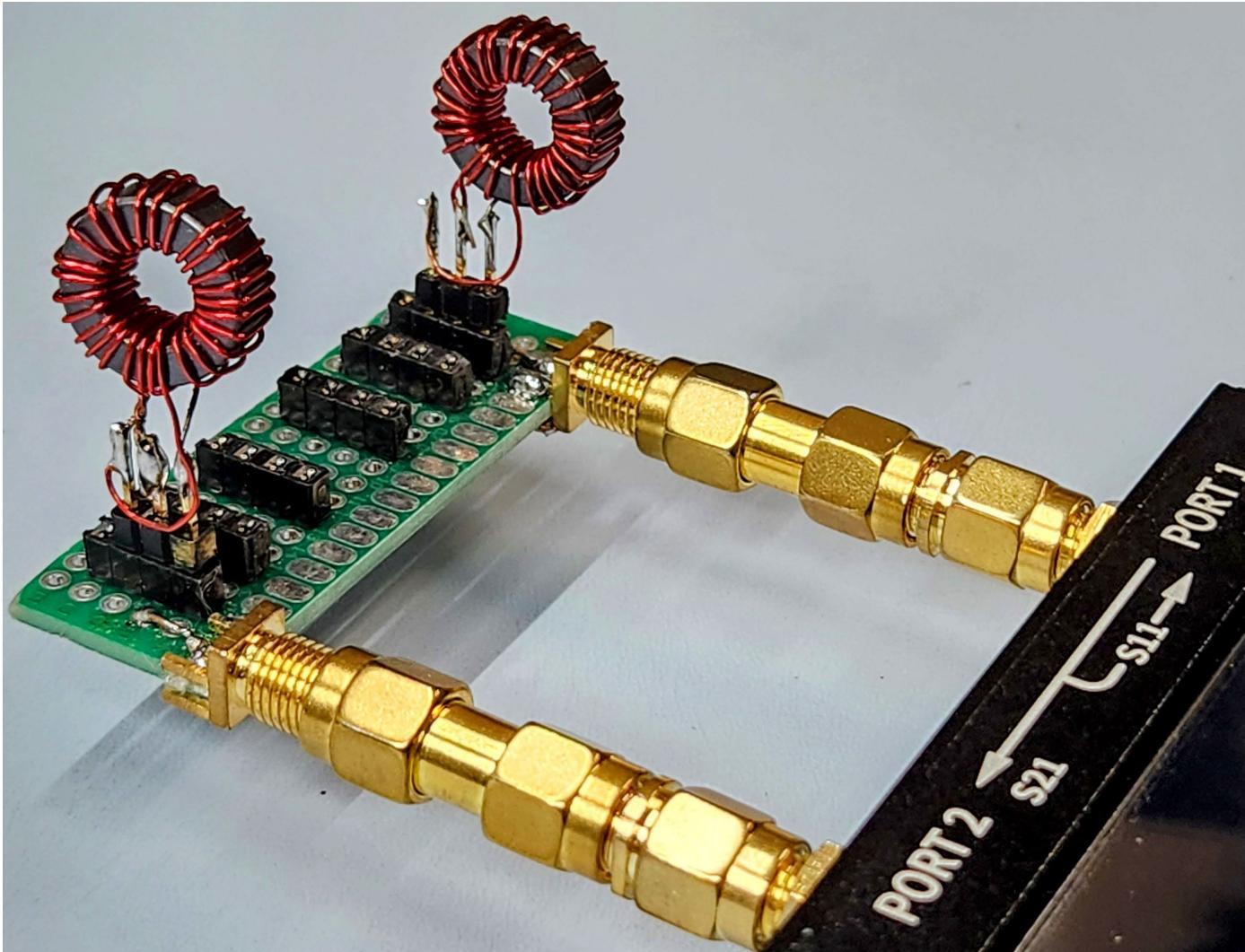

FT50-43 3:27 Back-to-Back

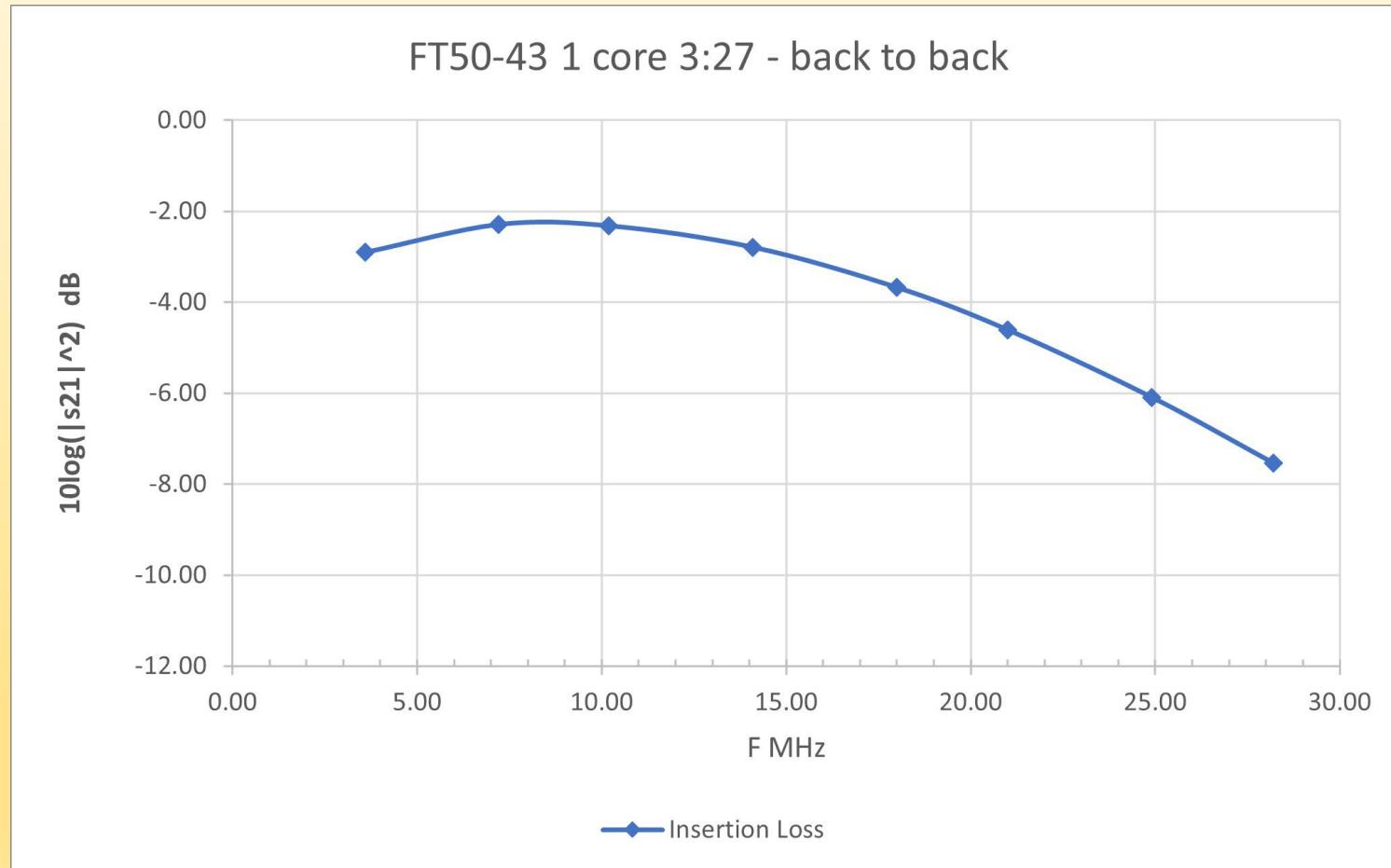


FT240-43 2 Cores 2:14 Back-to-Back

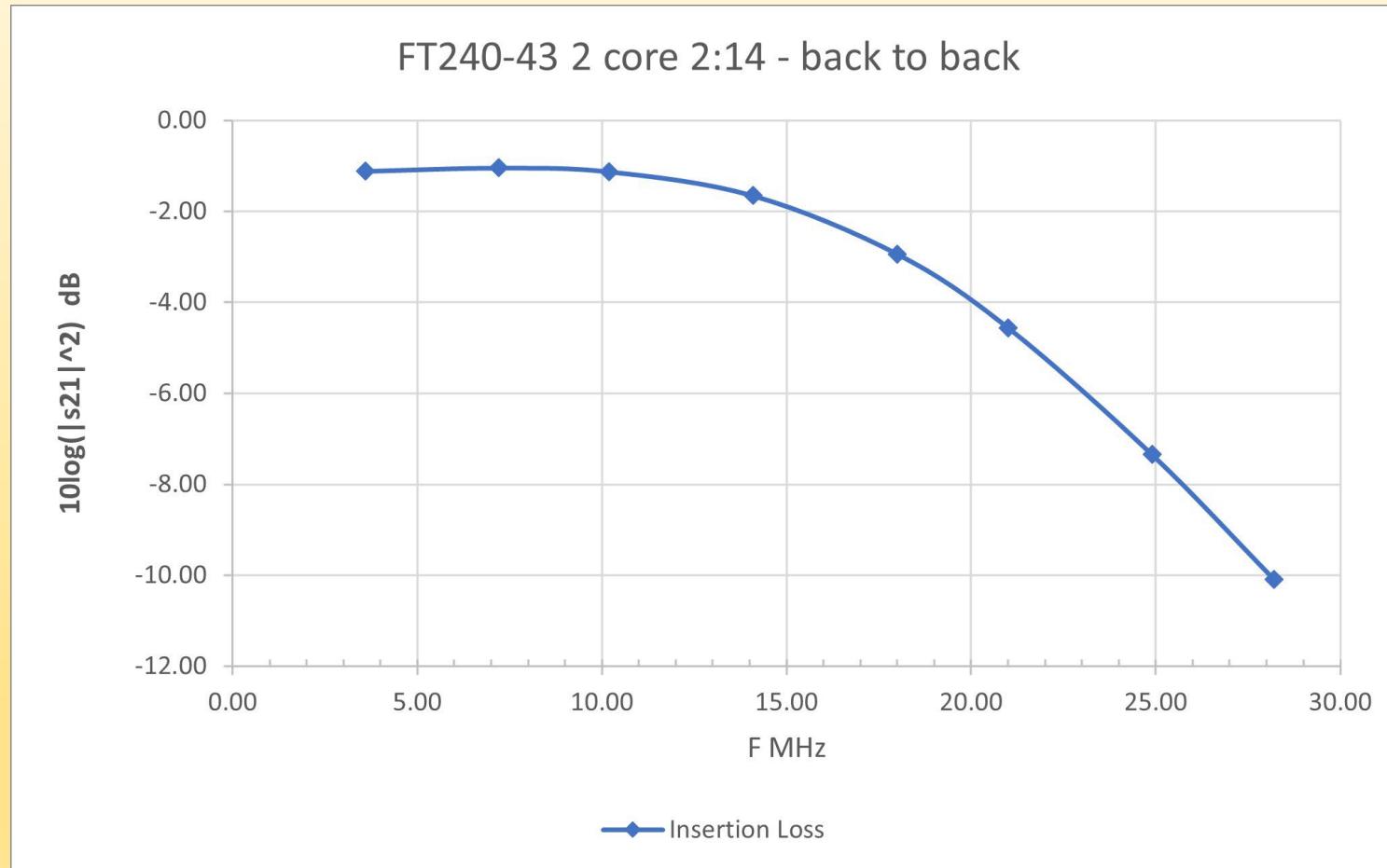

Transformer Loss Methods


- Loss Appear to Be Different From First Method
- Are They Equivalent?
- Let's Look at the Details
 - Schematic

Back-to-Back Transformers

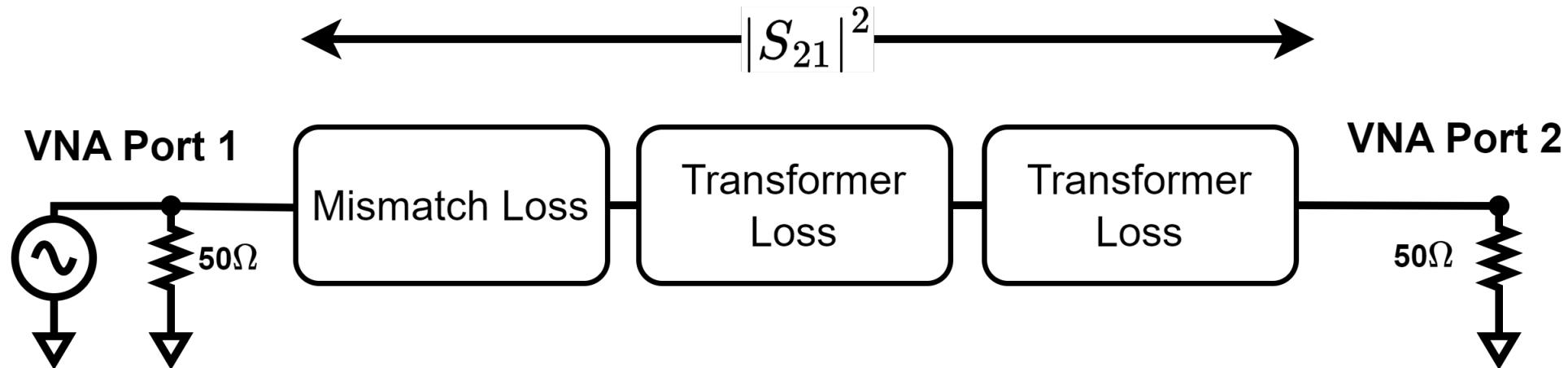

$$10 \log(|S_{21}|^2) = MM_{loss}(dB) + 2 \times \text{xfmr}_{loss}(dB)$$

Back-to-Back Transformers

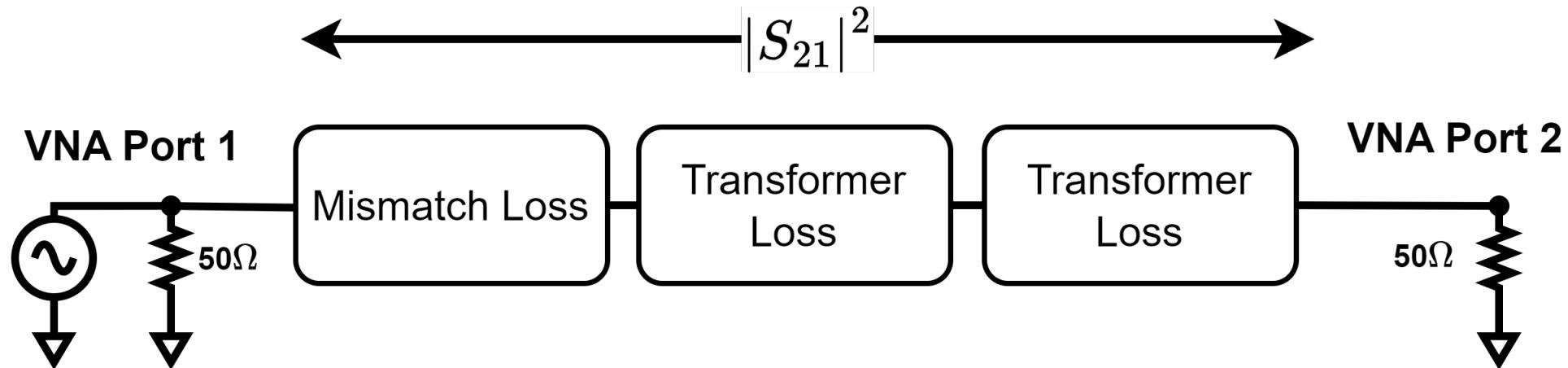

$$\text{xfmr}_{loss}(dB) = \left(10 \log(|S_{21}|^2) - MM_{loss}(dB) \right) / 2$$

Transformer Loss Equivalent Between Methods?

- Next Set of Measurements
 - Wind Two Identical Transformers
 - Characterize Each Individual Transformer
 - Single Transformer with Load - First Method
 - Transformer Loss


Transformer Loss Equivalent Between Methods?

- Characterize the Transformer Pair
 - Back-to-Back – Second Method
 - Insertion Loss
 - Mismatch Loss


Transformer Loss Equivalent Between Methods?

- Plot Each Set of Measurements
 - Transformer Loss From First Method
 - Insertion and Mismatch Difference
 - From Back-to-Back
 - $\left(10 \log(|S_{21}|^2) - MM_{loss}(dB)\right)/2$



Back-to-Back vs. Single Transformer

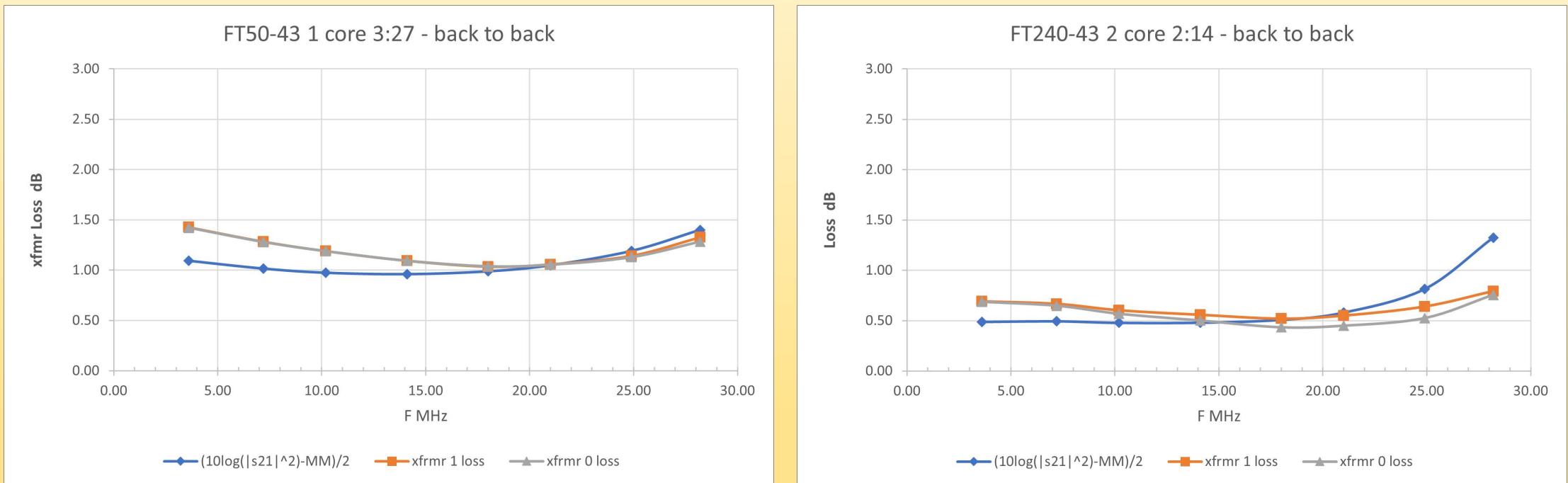



Primary Capacitor Reduces Insertion Loss

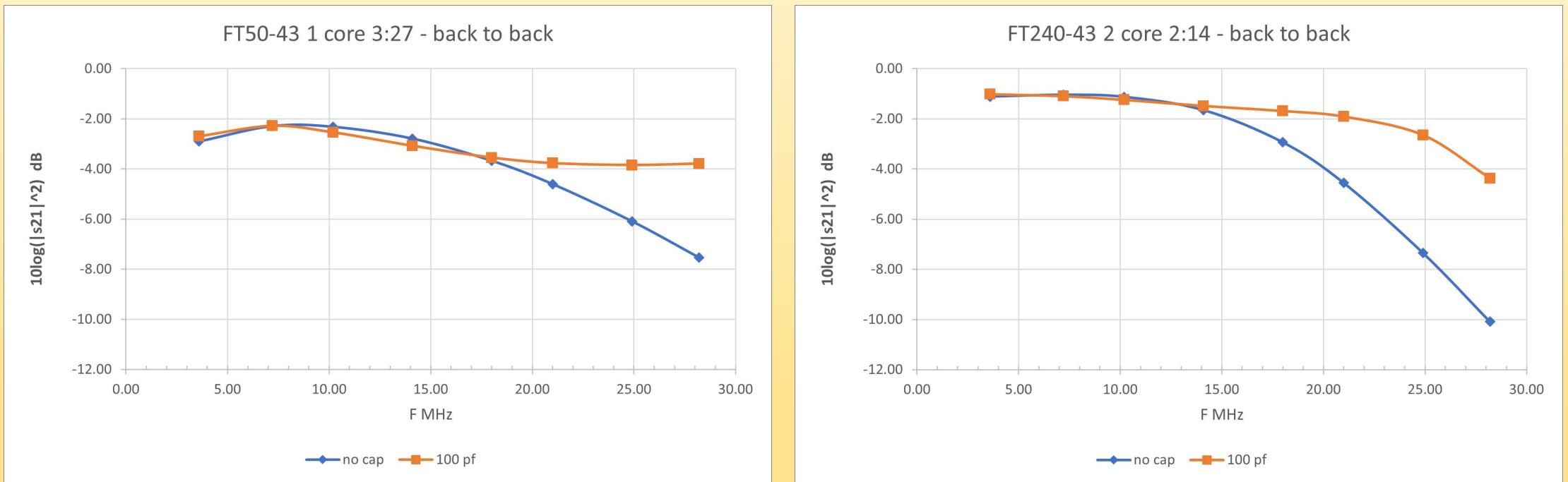

Primary Capacitor Reduces Mismatch Loss

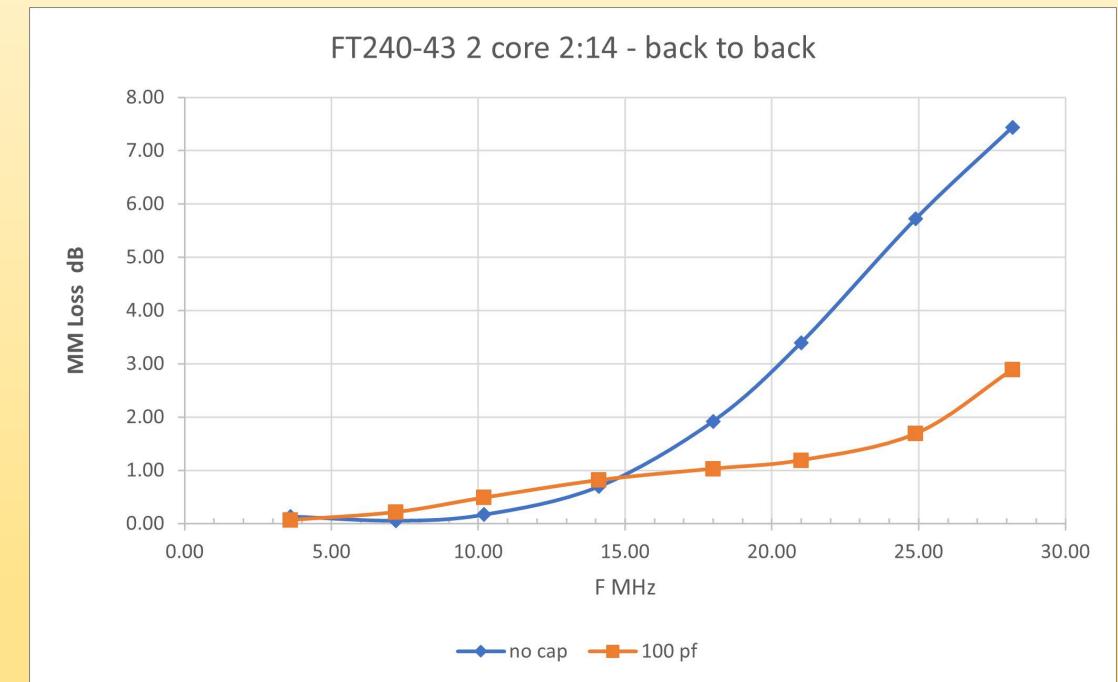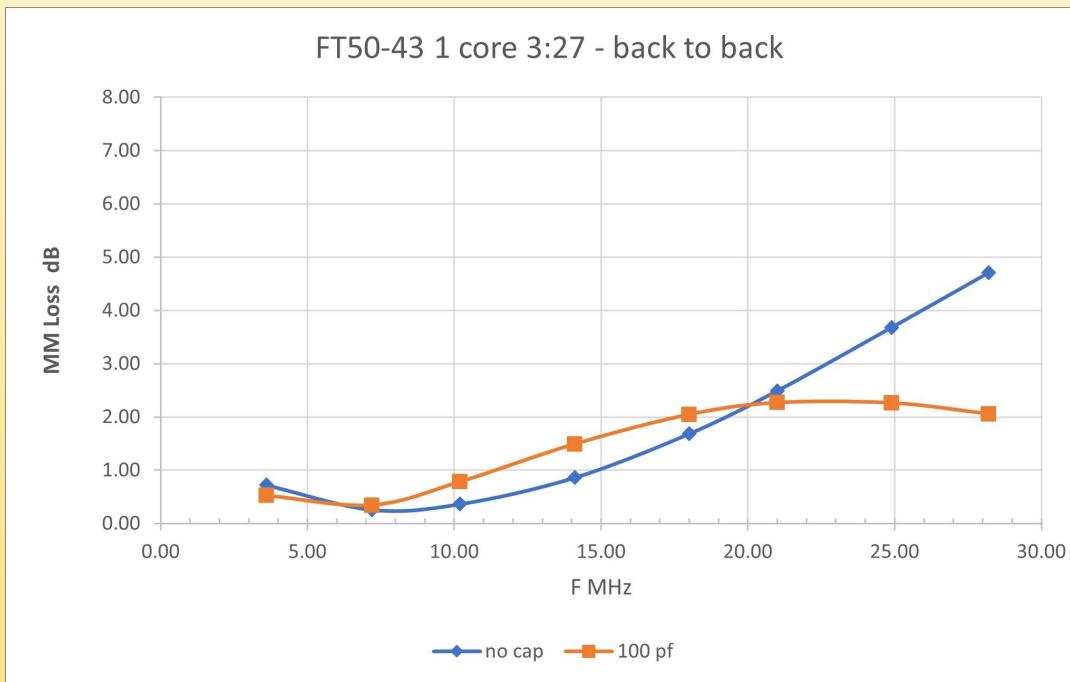

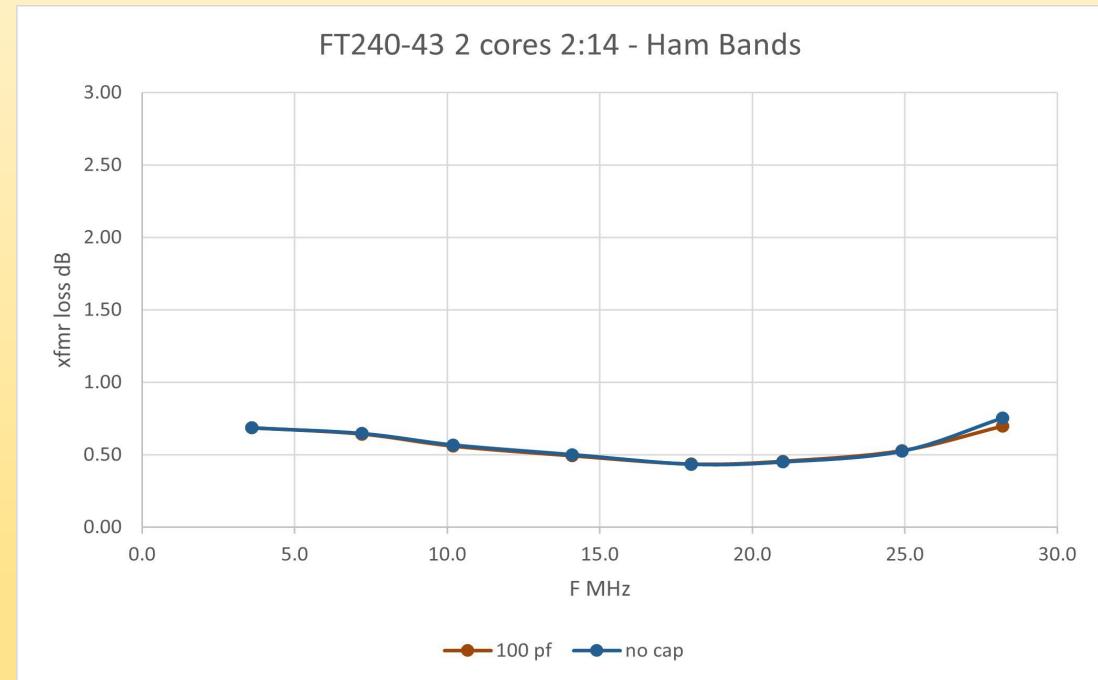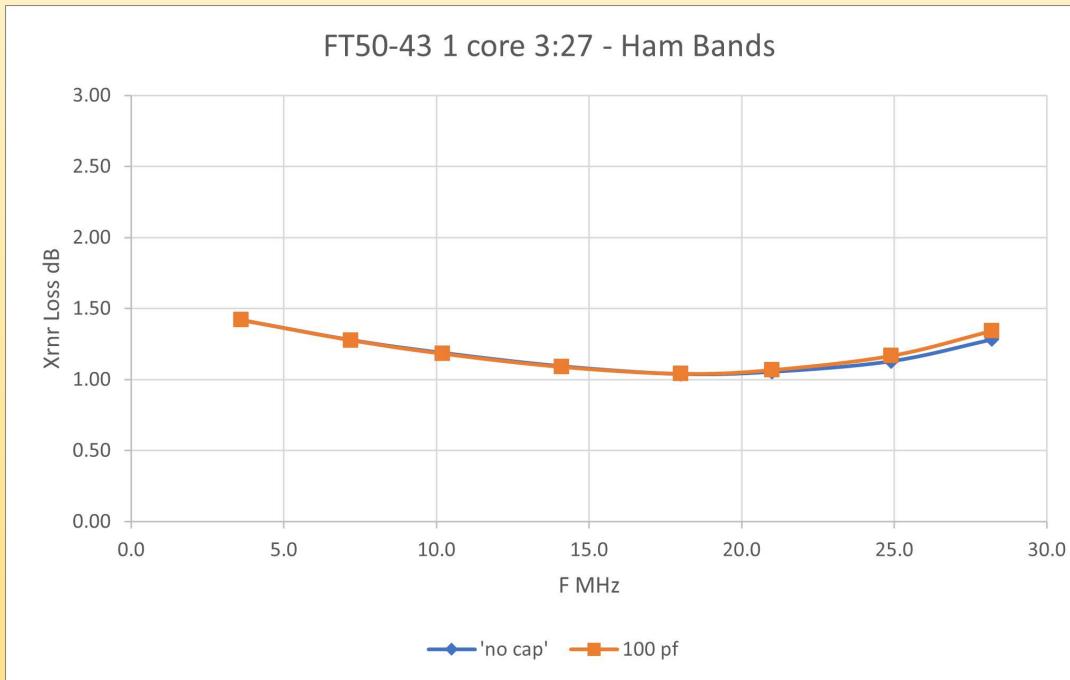Primary Capacitor Has Essentially No Affect on Transformer Loss



Back-to-Back Transformers

- Method Equivalence
 - General Agreement Between Methods
 - Mismatch Included in Back-to-Back
- Primary Capacitor
 - Reduces Mismatch Loss
 - Does Not Affect Core Loss

Method Comparison

Transformer plus Load

- Single Transformer
- Well Characterized Load Resistor
- Transformer and Mismatch Loss as Separate Data
- Calculations Required

Back-to-Back

- Two Transformers
- No Load Resistor
- Mismatch Loss Part of Result
- Few Calculations Needed

Measurement Considerations

- Test System Calibration
 - nanoVNA at Operating Temperature
 - Calibrate nanoVNA Attached to Test Fixture
 - Across Test Frequency Range
 - Short and Load on Header
 - 50Ω Load is SMD Like Load Resistor

Measurement Considerations

- Load Resistor
 - Measure Complex Impedance Across Test Frequency Range
 - In Test Fixture Position
 - SMD Mounted on Header

Measurement Considerations

- Transformer Loss is Sensitive to Measurement
 - Small Number That is a Difference of Two Much Larger Numbers (Insertion Loss and Load Loss)

$$\text{xfmr}_{loss}(dB) = 10 \log(|S_{21}|^2) - MM_{loss}(dB) - Load_{loss}(dB)$$

- Small Deviation in Measurement Values has a Large Effect on Transformer Loss


Small Deviation Produces Nonsensical Data

- Very Low Loss Transformers Difficult to Measure
- Test Procedure Important
- Limited by VNA Capabilities


Measured Values FT240-43 x2 2:14					$\Delta 1\% S_{11} S_{22} Z_{Load}$
Freq (MHz)	$10\log(S_{21} ^2)$ (dB)	Load_loss (dB)	xfmr_loss (dB)	xfmr_eff (%)	S_{11}
3.60	17.06	16.34	0.69	85.3	-0.15
7.20	17.10	16.32	0.67	85.8	-0.17
10.20	17.22	16.29	0.60	87.0	-0.23
14.10	17.58	16.21	0.56	87.9	-1.12
18.00	18.25	16.13	0.52	88.7	-1.15
21.00	18.97	16.03	0.55	88.1	-1.13
24.90	20.15	15.92	0.64	86.3	-1.03
28.20	21.31	15.80	0.79	83.3	-0.88

Transformer Loss Measurement Examples

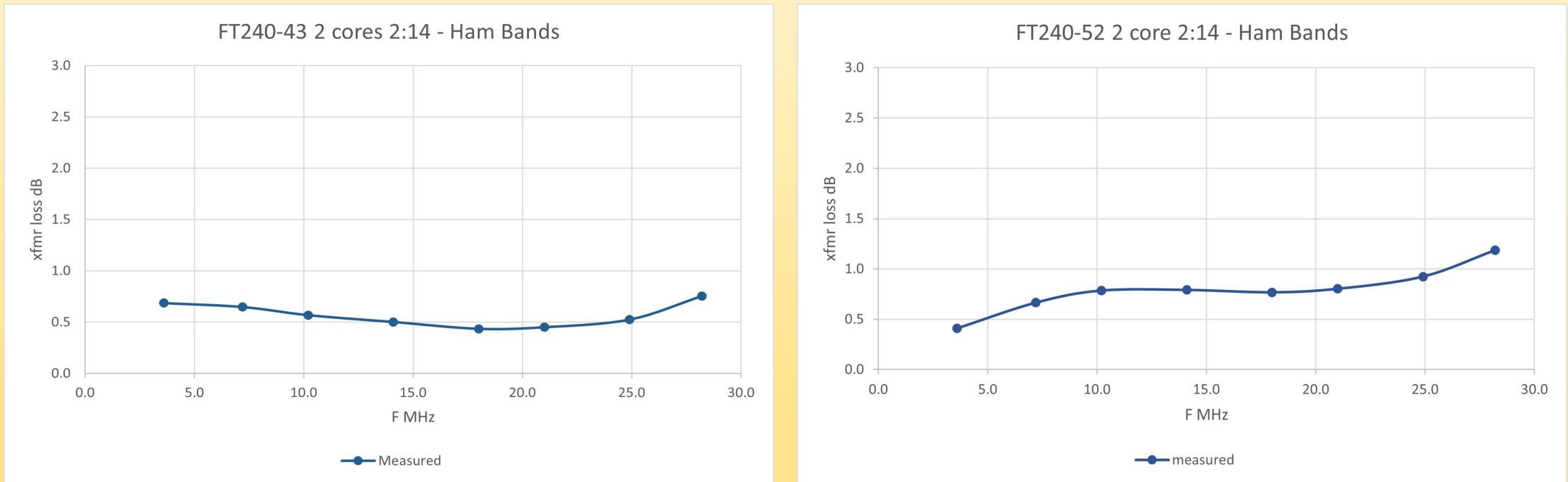
Transformer Loss: Comparing Material Type



Transformer Loss: Comparing # of Turns

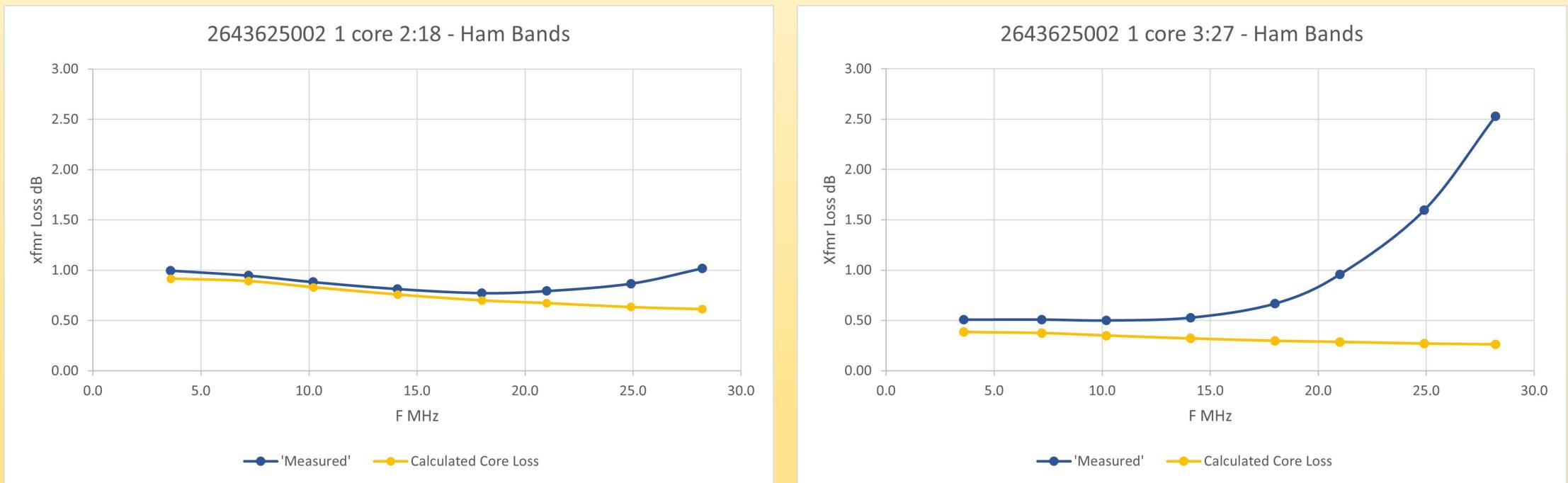

Transformer Loss: Comparing # of Turns

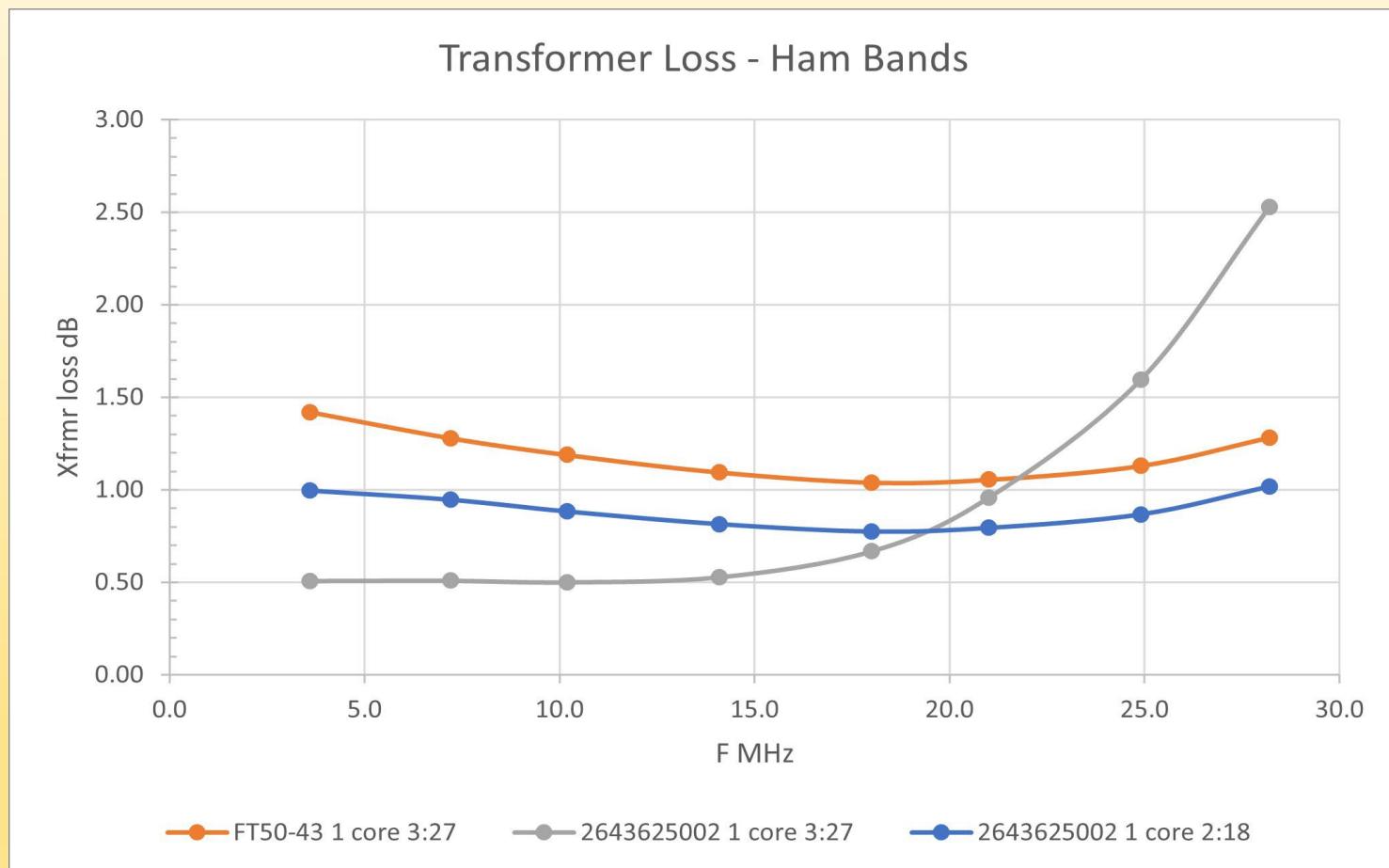

How Turns Affect Transformers

- More Turns Reduce Core Loss

$$\text{eff} = 1 - G_{cl}/G_s \quad R = 2\pi f N^2 A_l \left(\frac{\mu''}{\mu_i} \right)$$

- More Turns Increase High HF Band Transformer Loss
 - Winding Capacitance
 - Leakage Inductance
- Wide Bandwidth Transformers
 - Balance Higher Core Loss at Low HF for Lower Transformer Loss at High HF

Transformer Loss: Comparing Winding Style

- Conventional Wisdom
 - Primary is Twisted Over Secondary
 - Secondary Crossover after Seven Turns
 - Why?
- Should I Use This For My QRO Base Station?

49:1 Transformer

Primary 2 Turns.
Secondary 14 turns (Total turns)

To End Fed Half Wave Antenna.

Parts List

Toroid Core:
Mouser Part #623-5943003801
240-43 Toroid 12.7mm x 61mm

*Use 1, 2 or 3 cores depending on transmitter output to be used.

Capacitor:
Mouser Part #81-DHR4E4C221K2BB
100 - 110 pF. You can use TWO 220 pF @ 15 KV in series.

Antenna:
80m - 10m use a 134' wire.
40m - 10m use a 67' wire, etc.


Wire:
14 gauge enameled wire. **

** When using 3 toroid cores start with a Primary wire of ~13" and Secondary of ~80" long. 1 & 2 cores will use less wire.


To TX Gnd.

Revised: 07/14/2017 - K1TA

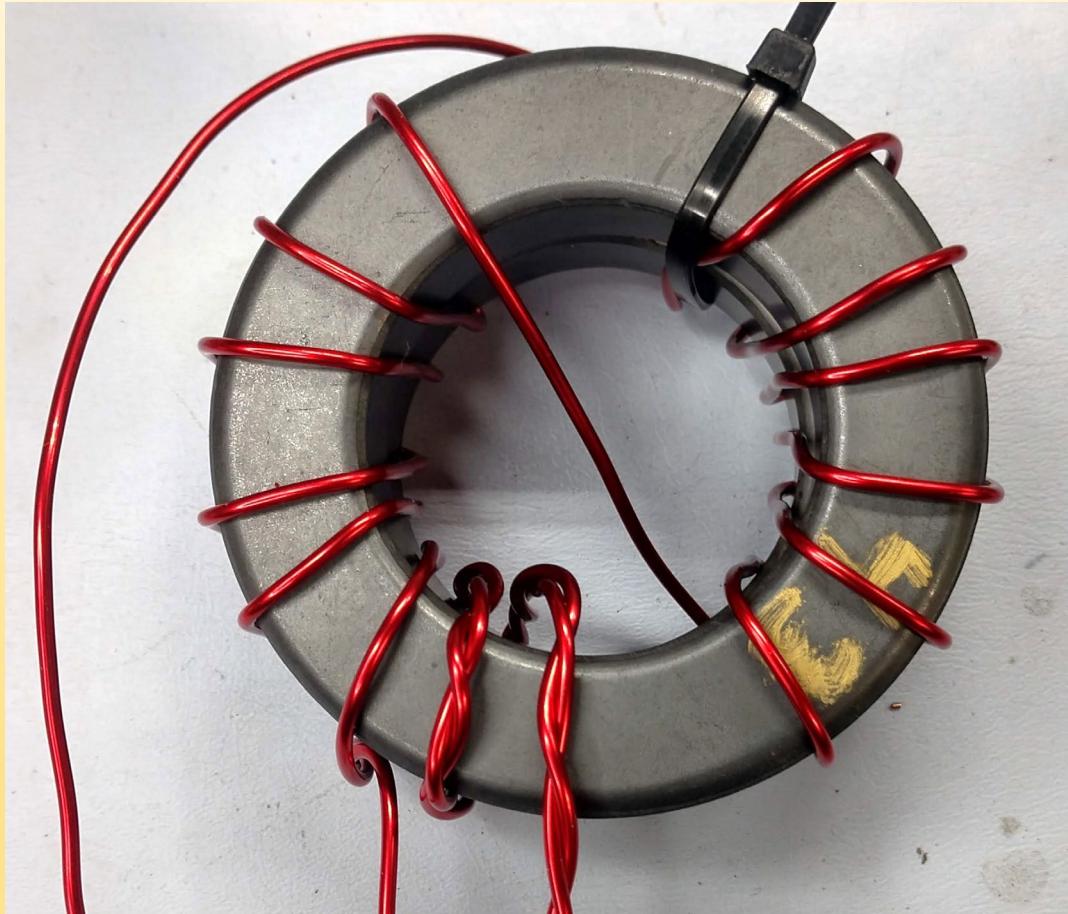Transformer Loss: Comparing Winding Style




Twisted Primary with Crossover

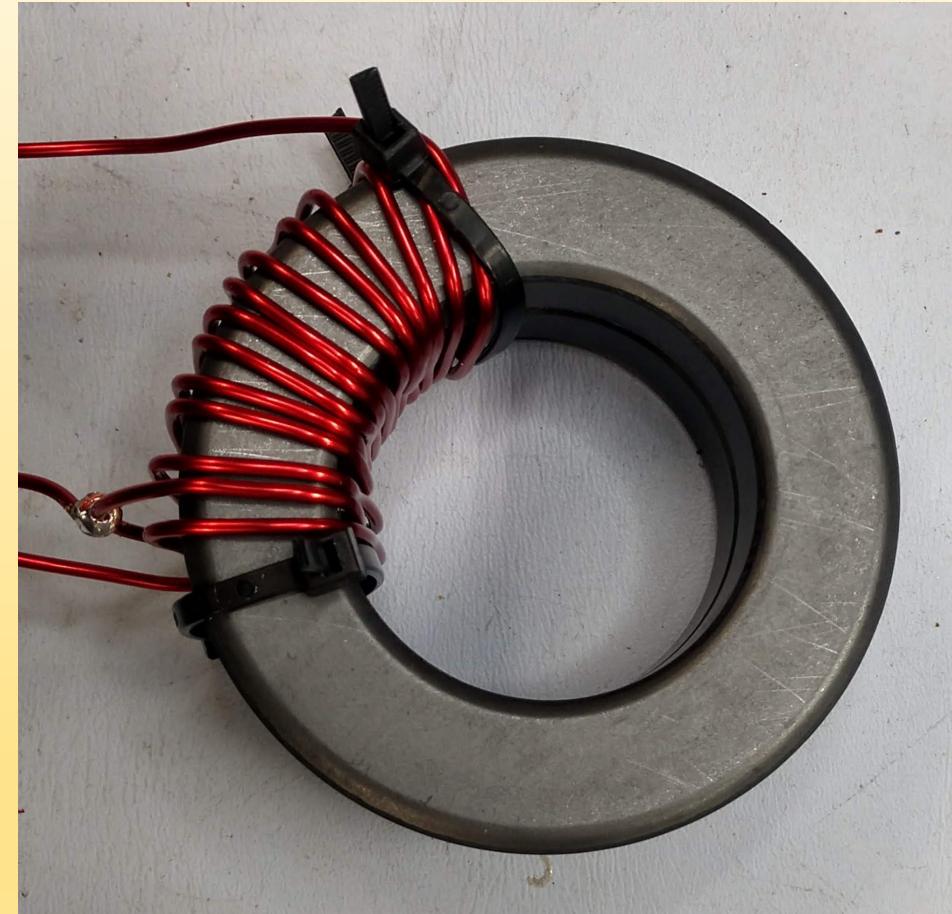


Tapped Single Winding

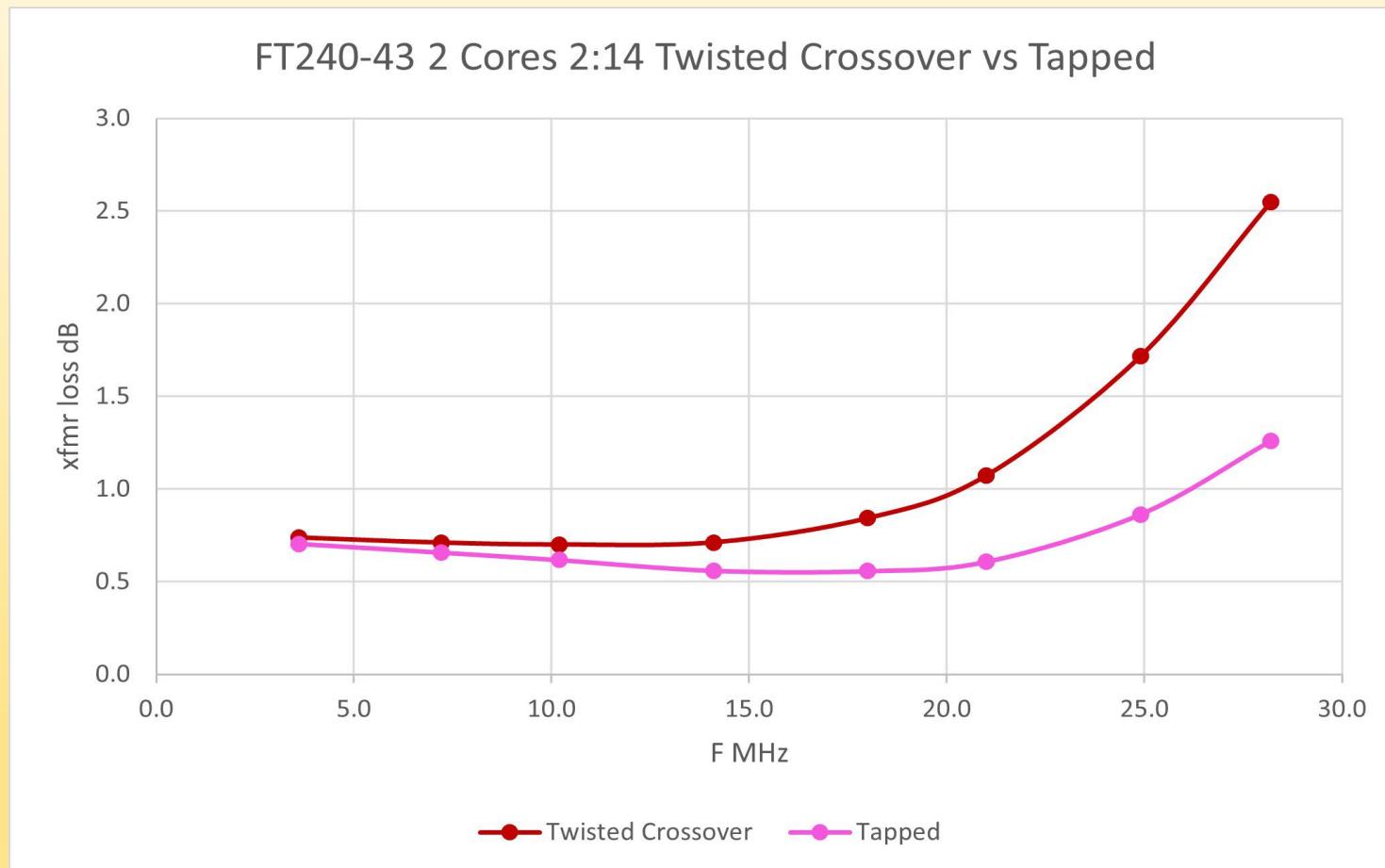Transformer Loss: Comparing Winding Style



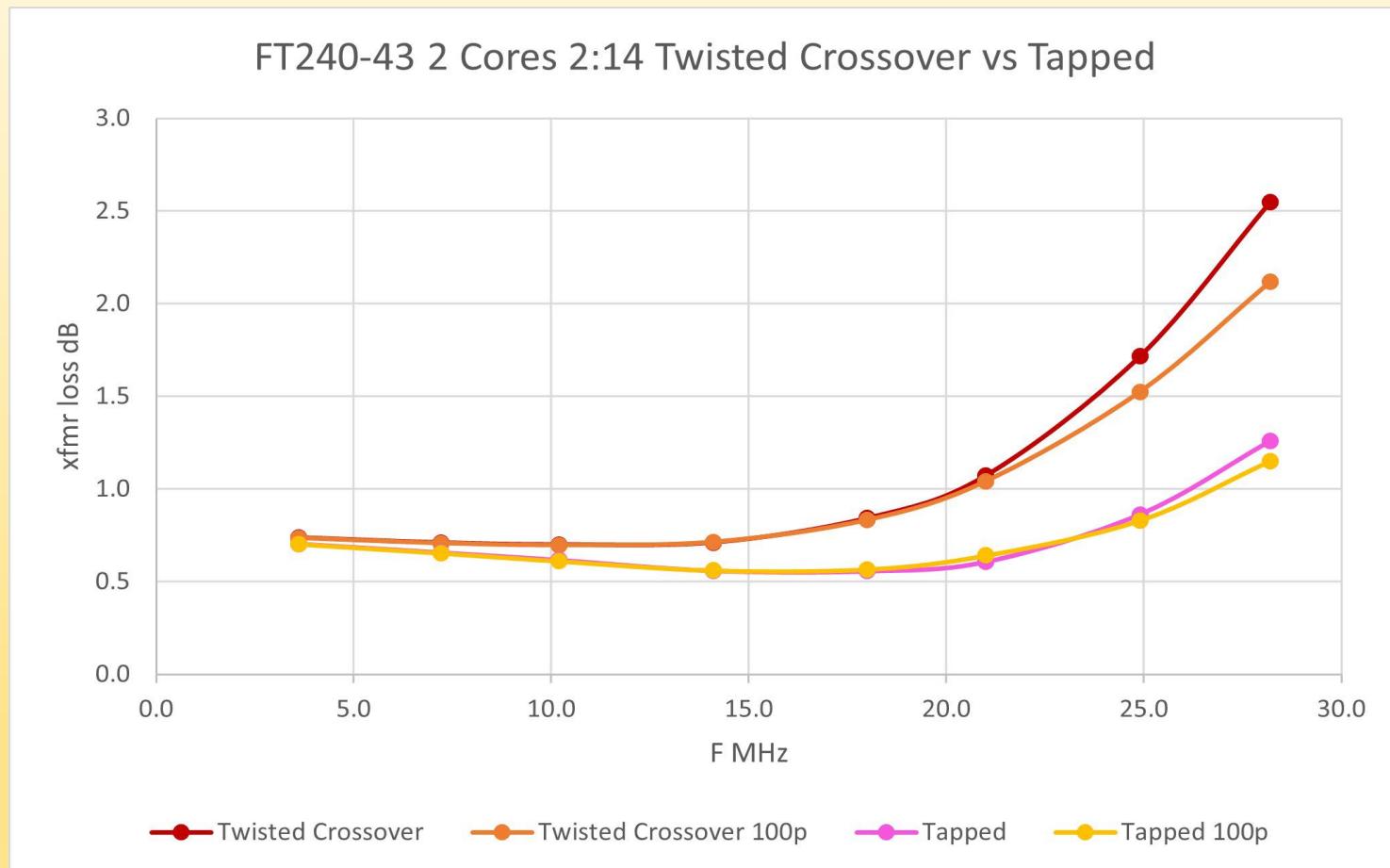Transformer Loss: Comparing Winding Style



Transformer Loss: Comparing Winding Style



What We Learned

- Ferrite Core Characteristics Vary With Frequency
- Ferrite Cores Have Real Resistance – Core Loss
 - Power Loss and Heat
- Two Methods to Measure Transformer Loss
- Core Loss Can be a Good Estimate for HF Transformer Loss
- Transformer Loss is Sensitive to Measurement
- Transformer Loss Measurement is Fun -> Try It!

References

- <https://www.ai6xg.com/post/evaluating-efficiency-transformer-and-mismatch-losses-in-toroid-transformers-some-observations>
- <https://www.ai6xg.com/post/reactive-component-measurement-with-the-nanovna>
- <https://github.com/phase2682/FC-XFMRS-AI6XG>
- A method for estimating the impedance of a ferrite cored toroidal inductor at RF – Owen Duffy
- <https://owenduffy.net/calc/toroid.htm>
- <https://owenduffy.net/calc/toroid2.htm>